

**CS221: Digital Design**

# **FSM State Encoding**

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

# Encoding

- What is State encoding?
- Random Encoding
- Sequential Encoding
- Gray Encoding
- One Hot Encoding
- Output Oriented Encoding
- Heuristics for Encoding


# **State Encoding/Assignment**

# State assignment

- State encoding:
  - Assigning unique binary value to each state
  - So that we can implement FSM
- Since we don't care about the actual flip-flop values for each state
- We can assign each state to any binary number we like **as long as**
  - Each state is assigned a unique binary number
 
# Example of FSM: 3 cycle Laser

- Require 4 States
- Assigning unique binary value/code to each state
- Options available : 4!



# State Encoding Example

- Four state FSM: S0, S1, S2, S3 : 4! options

SL	S0	S1	S2	S3
1	00	01	10	11
2	00	01	11	10
3	00	10	01	11
4	00	10	11	01
5	00	11	01	10
6	00	11	10	01
7	01	00	11	10
8	01	00	10	11
9	01	10	11	00
10	01	10	00	11
11	01	11	10	00
12	01	11	00	11

SL	S0	S1	S2	S3
13	10	01	00	11
14	10	01	11	00
15	10	00	01	11
16	10	00	11	01
17	10	11	01	00
18	10	11	00	01
19	11	00	01	10
20	11	00	10	01
21	11	10	01	00
22	11	10	00	01
23	11	01	10	00
24	11	01	00	11

## State assignment

- Since we don't care about the actual flip-flop values for each state we can assign each state to any binary number we like **as long as** each state is assigned a unique binary number
- Suppose a FSM have 6 states: Modulo 6 Counter
- If we use 3 bits to encode the 6 states, we have

$$\binom{8}{6} = \frac{8!}{6!(8-6)!}$$

possible choosing the 6 states from 8 total state

– Than encodings

# State Encoding

- The cost & delay of FSM implementation depends on encoding of symbolic states.
  - e.g., 4 states can be encoded in  $4! = 24$  different ways
- There are more than  $n!$  different encodings for  $n$  states.
  - **Exploration of all encodings is impossible,** therefore heuristics are used
- Heuristics Used
  - One-hot encoding, Minimum-bit change, Prioritized adjacency



## State assignment

state	Encoding 1 (binary)	Encoding 2 (Gray)	Encoding 3
a	000	000	000
b	001	001	100
c	010	011	010
d	011	010	101
e	100	110	011

# State Encoding

- Binary and Gray encoding use the minimum number of bits for state register
- Gray and Johnson code: Two adjacent codes differ by only one bit
  - Reduce simultaneous switching
  - Reduce crosstalk, Reduce glitch

# One-hot encoding

- One flip-flop per state encoding
- Leads to greater number of flip-flops than binary encoding but possibly to simpler logic

# State Assignment Problem

- Some state assignments are better than others.
- The state assignment influences the complexity of the state machine.
  - The combinational logic required in the state machine design is dependent on the state assignment.
- Types of state assignment
  - Binary encoding:  $2^N$  states  $\rightarrow$  N Flip-Flops
  - Gray-code encoding:  $2^N$  states  $\rightarrow$  N Flip-Flops
  - One-hot encoding: N states  $\rightarrow$  N Flip-Flops

# FSM: State Assignment

## Example

Design a FSM that detects a sequence of two or more consecutive ones on an input bit stream.


The FSM should output a 1 when the sequence is detected, and a 0 otherwise.

# FSM: State Assignment

Input:        0 1 1 1 0 1 0 1 1 0 1 1 1 0 1 ...

Output:      0 0 1 1 0 0 0 0 1 0 0 1 1 0 0 ...

# FSM: State Assignment

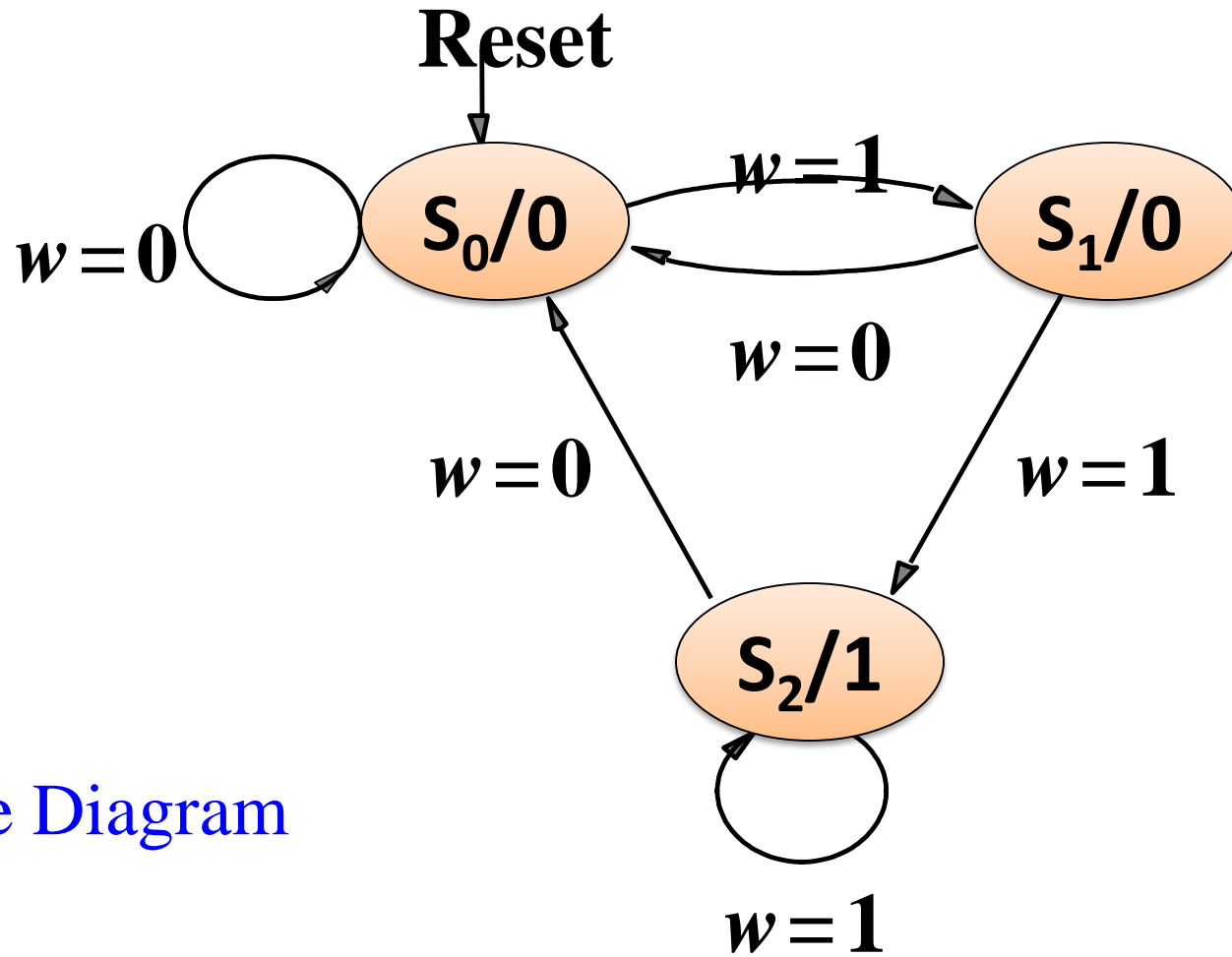

State Diagram

# FSM: State Assignment

Present State	Next State		Output
	w = 0	w = 1	
$S_0$	$S_0$	$S_1$	0
$S_1$	$S_0$	$S_2$	0
$S_2$	$S_0$	$S_2$	1

State Table



# FSM: State Assignment #1

## State Assigned Table

Present State			Next State						Output
			w = 0			w = 1			
	$Q_A$	$Q_B$		$Q_A^+$	$Q_B^+$		$Q_A^+$	$Q_B^+$	z
$S_0$	0	0	$S_0$	0	0	$S_1$	0	1	0
$S_1$	0	1	$S_0$	0	0	$S_2$	1	0	0
$S_2$	1	0	$S_0$	0	0	$S_2$	1	0	1
	1	1		d	d		d	d	d

Using Binary Encoding  
for the State Assignment

$$\begin{aligned}D_B &= wQ'_A Q'_B \\D_A &= w(Q_A + Q_B) \\Z &= Q_A\end{aligned}$$

# FSM: State Assignment #2

## State Assigned Table

Present State			Next State						Output
			w = 0			w = 1			
	$Q_A$	$Q_B$		$Q_A^+$	$Q_B^+$		$Q_A^+$	$Q_B^+$	z
$S_0$	0	0	$S_0$	0	0	$S_1$	0	1	0
$S_1$	0	1	$S_0$	0	0	$S_2$	1	1	0
$S_2$	1	1	$S_0$	0	0	$S_2$	1	1	1
	1	0		d	d		d	d	d

$$D_A = w \cdot Q_B$$

$$D_B = w$$

$$Z = Q_A$$

Using Gray-code Encoding  
for the State Assignment

# FSM: State Assignment #3

State Assigned Table

Present State				Next State							
				w = 0				w = 1			
	$Q_A$	$Q_B$	$Q_C$		$Q_A^+$	$Q_B^+$	$Q_C^+$		$Q_A^+$	$Q_B^+$	$Q_C^+$
$S_0$	0	0	1	$S_0$	0	0	1	$S_1$	0	1	0
$S_1$	0	1	0	$S_0$	0	0	1	$S_2$	1	0	0
$S_2$	1	0	0	$S_0$	0	0	1	$S_2$	1	0	0

Using One-hot Encoding  
for the State Assignment


For each state only one flip-flop is set to 1.  
The remaining combination of state  
variables are not used.

$$\begin{aligned} D_A &= w \cdot Q_C' \\ D_B &= w \cdot Q_C \\ D_C &= w' \end{aligned}$$

# State Encoding

#	Binary	Gray	Johnson	One-hot
0	000	000	0000	00000001
1	001	001	0001	00000010
2	010	011	0011	00000100
3	011	010	0111	00001000
4	100	110	1111	00010000
5	101	111	1110	00100000
6	110	101	1100	01000000
7	111	100	1000	10000000

# Johnson Counter

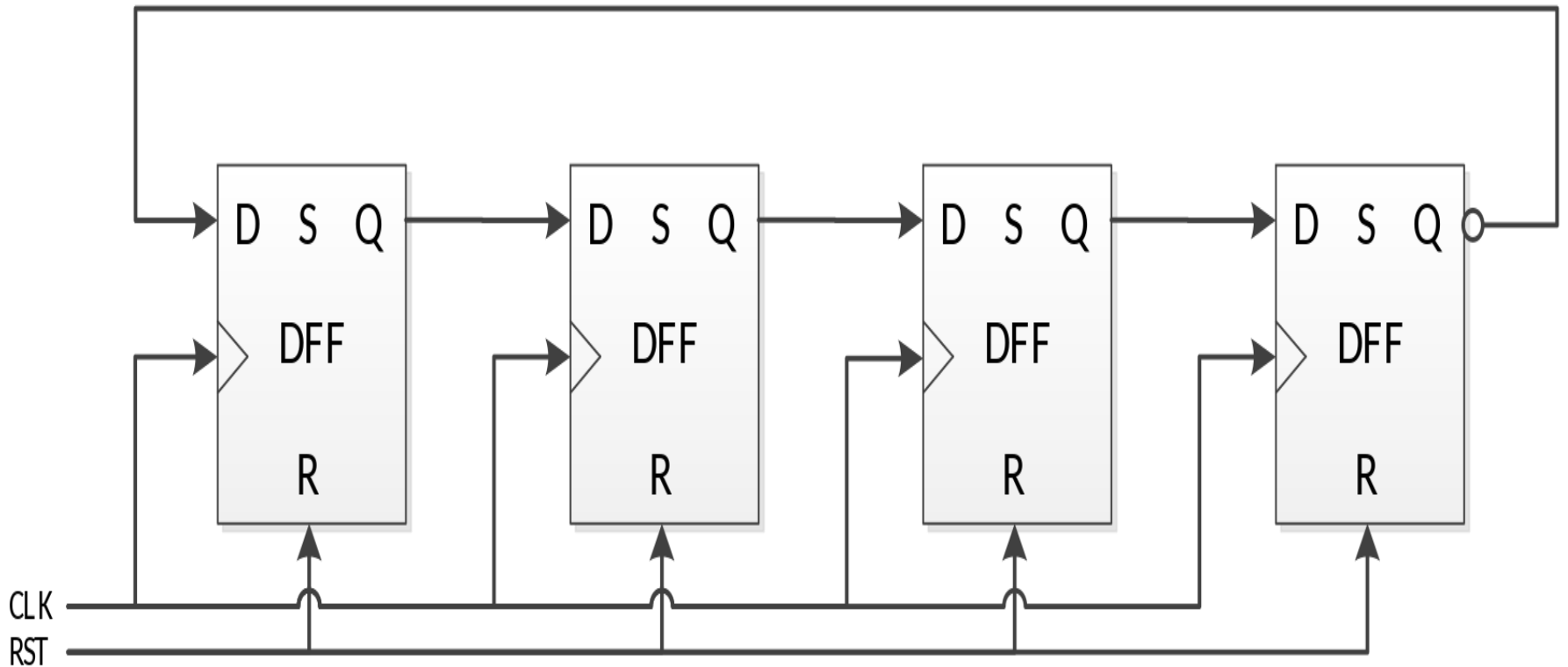


# State Encoding

- The cost & delay of FSM implementation depends on encoding of symbolic states.
  - e.g., 4 states can be encoded in  $4! = 24$  different ways
- There are more than  $n!$  different encodings for  $n$  states.
  - **Exploration of all encodings is impossible,** therefore heuristics are used
- Heuristics Used
  - One-hot encoding, Minimum-bit change, Prioritized adjacency
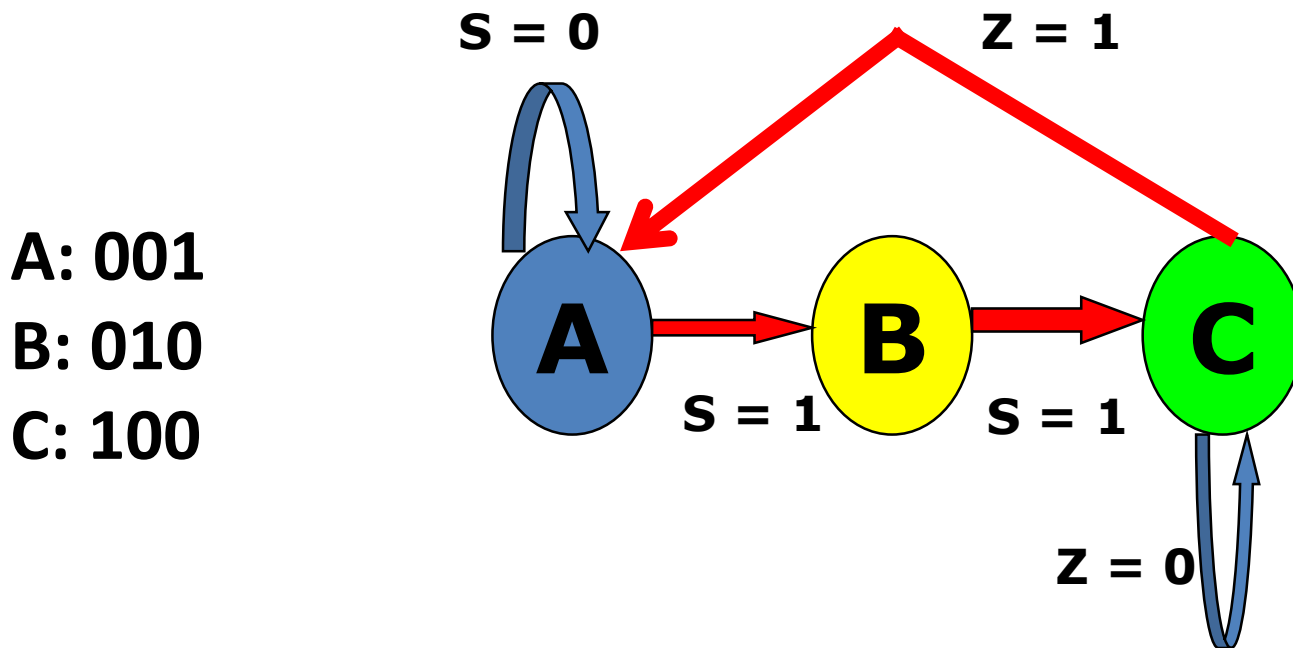
# One-hot Encoding

- Uses redundant encoding in which one flip-flop is assigned to each state.
- Each state is distinguishable by its own flip-flop having a value of 1 while all others have a value of 0.




# Minimum-bit Change

- Assigns codes to states so that
  - The total number of **bit changes** for all state transitions **is minimized**.
- In other words, if every arc in the state diagram has a **weight**
  - That is equal to the **number of bits** by which the source and destination encoding **differ**
  - This strategy would select the one that **minimizes the sum** of all these weights.




# Minimum-bit Change

Encoding with  
6 bit changes

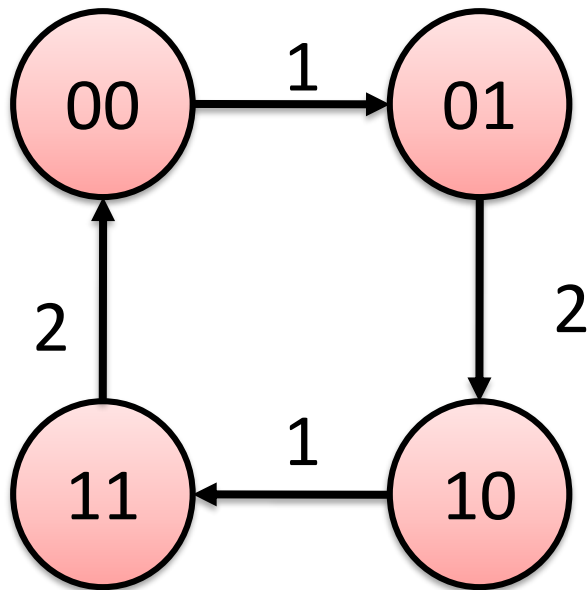

Straight-forward  
sequential Encoding

Encoding with  
4 bit changes

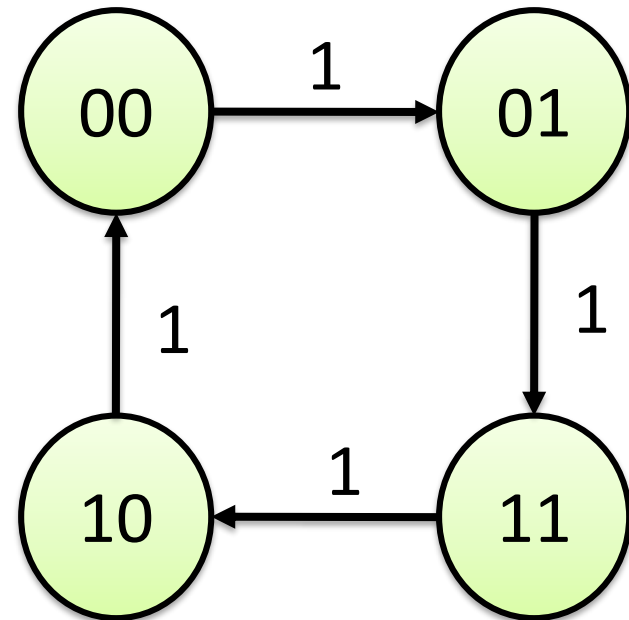


Minimum Bit  
Change Encoding
 
# The Idea of Adjacency

- Inputs are A and B
- State variables are Y1 and Y2
- An output is  $F(A, B, Y1, Y2)$  or  $F(Y1, Y2)$
- A next state function is  $G(A, B, Y1, Y2)$

*Karnaugh map of  
output function or  
next state function*




- Larger clusters produce smaller logic function.
- Clustered minterms differ in one variable.

# Size of an Implementation

- Number of **product terms** determines number of **gates**.
- Number **of literals** in a product term determines number of gate **inputs**, which is proportional to number of transistors.
- Hardware area proportional to total number of literals
- Examples of four minterm functions:
  - **F1** =  $ABCD + A'B'C'D' + A'B'CD + A'B'CD$  has **16 literals**
  - **F2** =  $ABC + A'C'D$  has **6 literals**

 
# Rule 1 (Priority #1), Common Dest

States that have the same next state for some fixed input should be assigned logically adjacent codes.


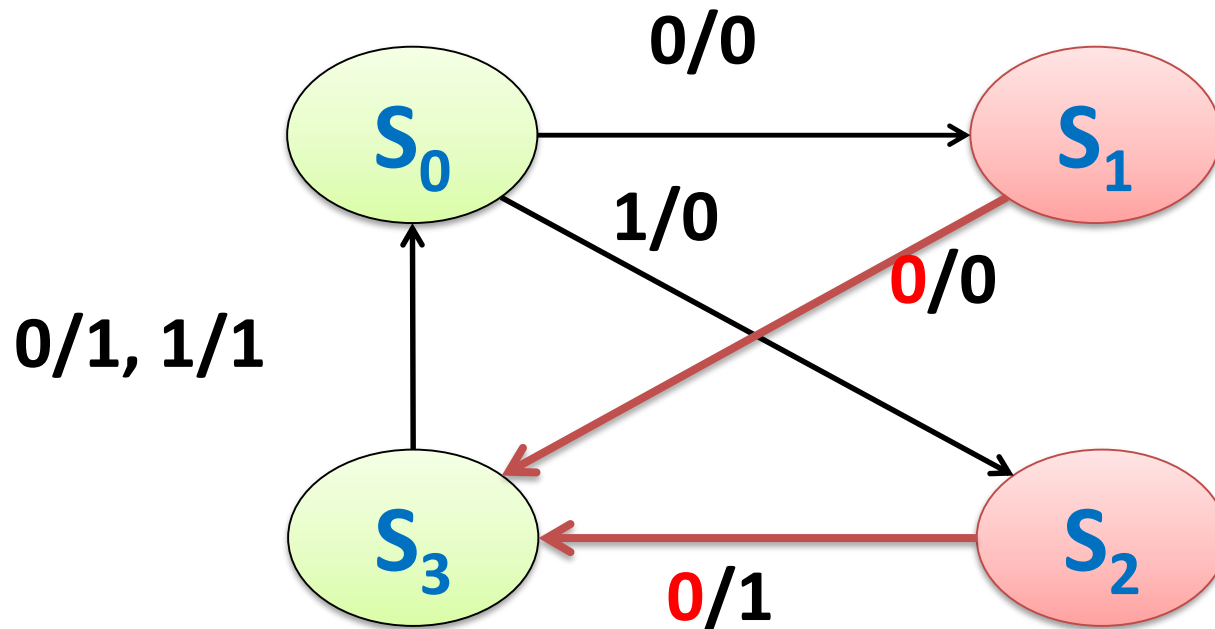
# Rule 1 (Priority #1), Common Dest

States that have the same next state for some fixed input should be assigned logically adjacent codes.




**Rule #1: ( $S_1, S_2$ )**

**The input value of 0 will move both states into the same state  $S_3 \Rightarrow \text{Adj}(S_1, S_2)$**

 
# Rule 2 (Priority #2), A Common Source

States that are the next states of the same state under logically adjacent inputs, should be assigned logically adjacent codes.


 
# Rule 2 (Priority #2), A Common Source

States that are the next states of the same state under logically adjacent inputs, should be assigned logically adjacent codes.




**Rule #2: ( $S_1, S_2$ )**

**They are both next states of the state  $S_0 \rightarrow \text{Adj}(S_1, S_2)$**
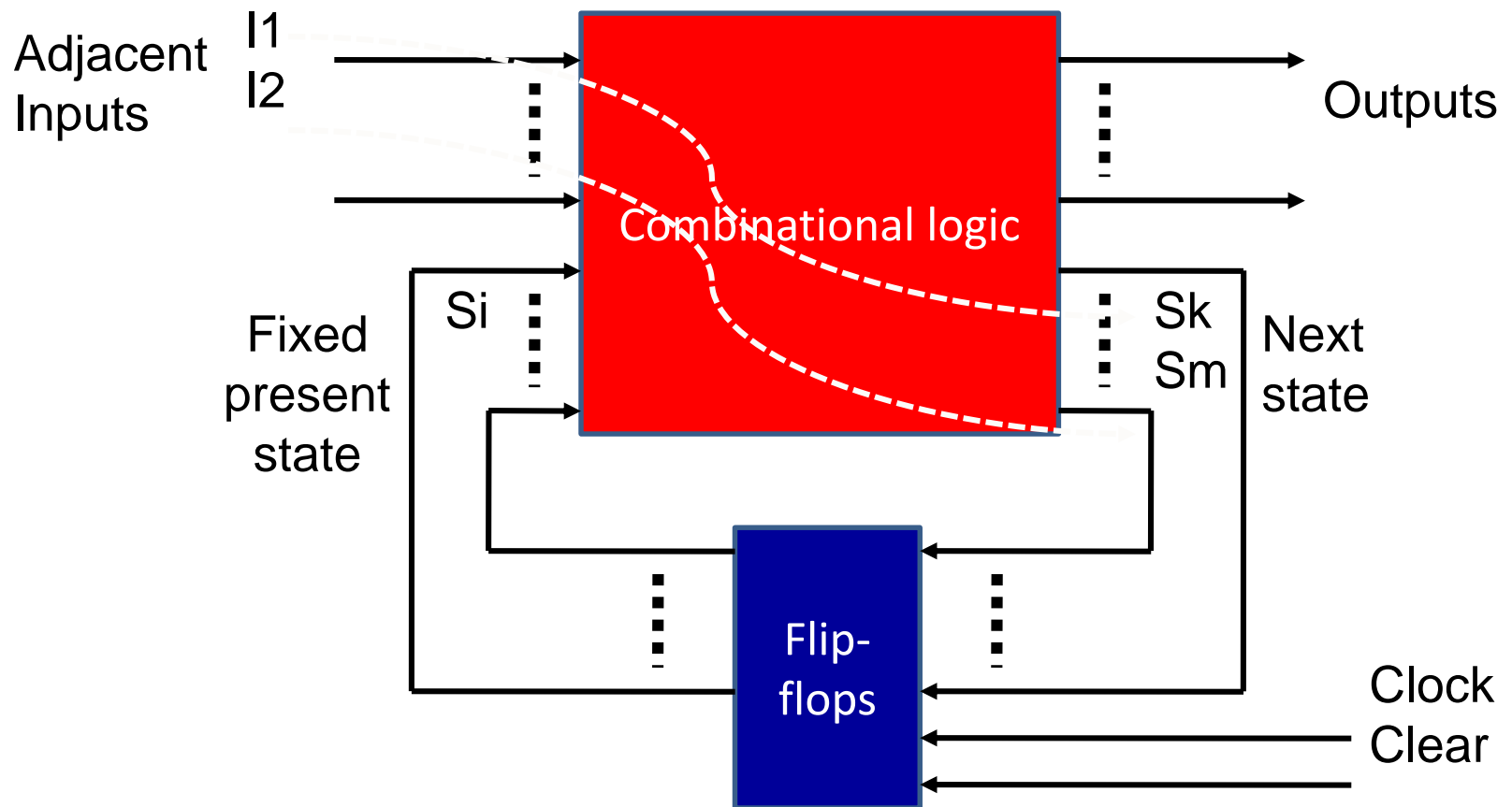
# Rule 3 (Priority #3), A Common Output


States that have the same output value for the same input value, should be assigned logically adjacent codes.




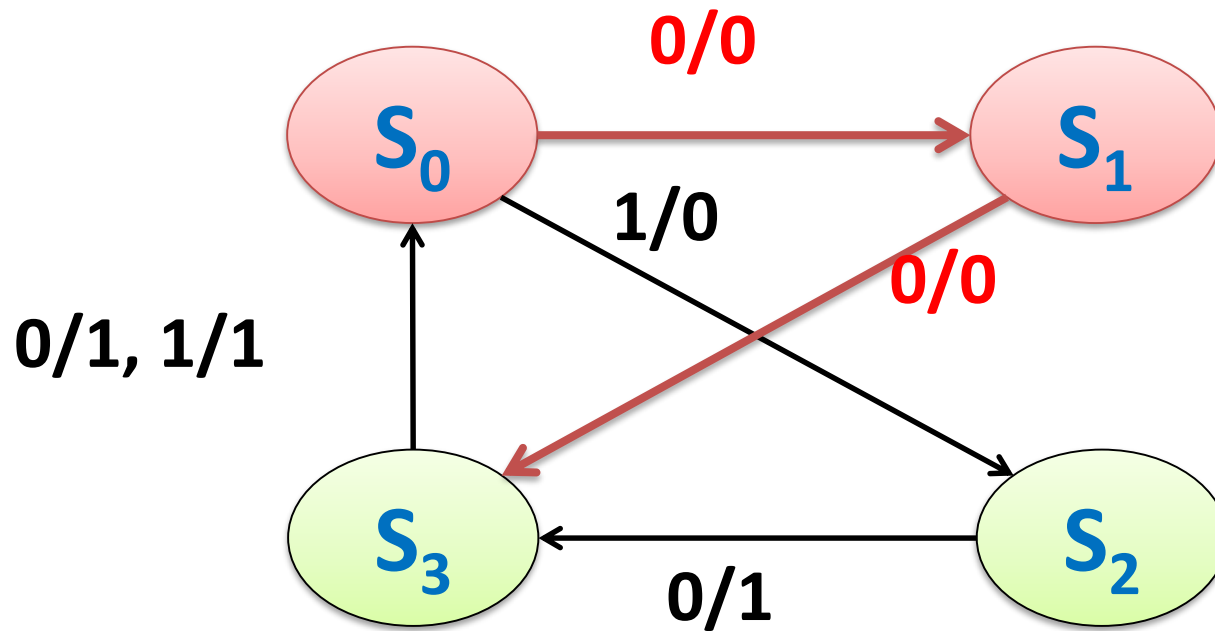
# Rule 3 (Priority #3), A Common Output


States that have the same output value for the same input value, should be assigned logically adjacent codes.



**Rule #3: ( $S_0, S_1$ ):** states  $S_0$  and  $S_1$  have the same output value 0 for the same input value 0  $\rightarrow$  Adj ( $S_0, S_1$ )
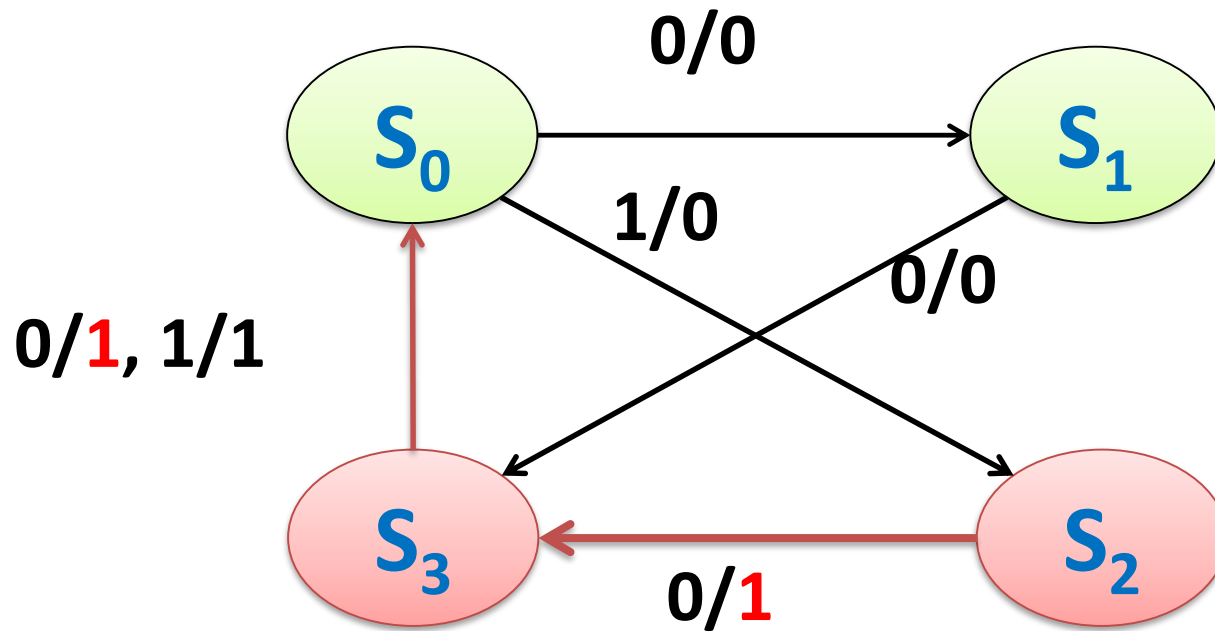
# Rule 3 (Priority #3), A Common Output


States that have the same output value for the same input value, should be assigned logically adjacent codes.



**Rule #3: ( $S_2, S_3$ ), states  $S_2$  and  $S_3$  have the same output value 1 for the same input value 0  $\rightarrow$  Adj ( $S_2, S_3$ )**

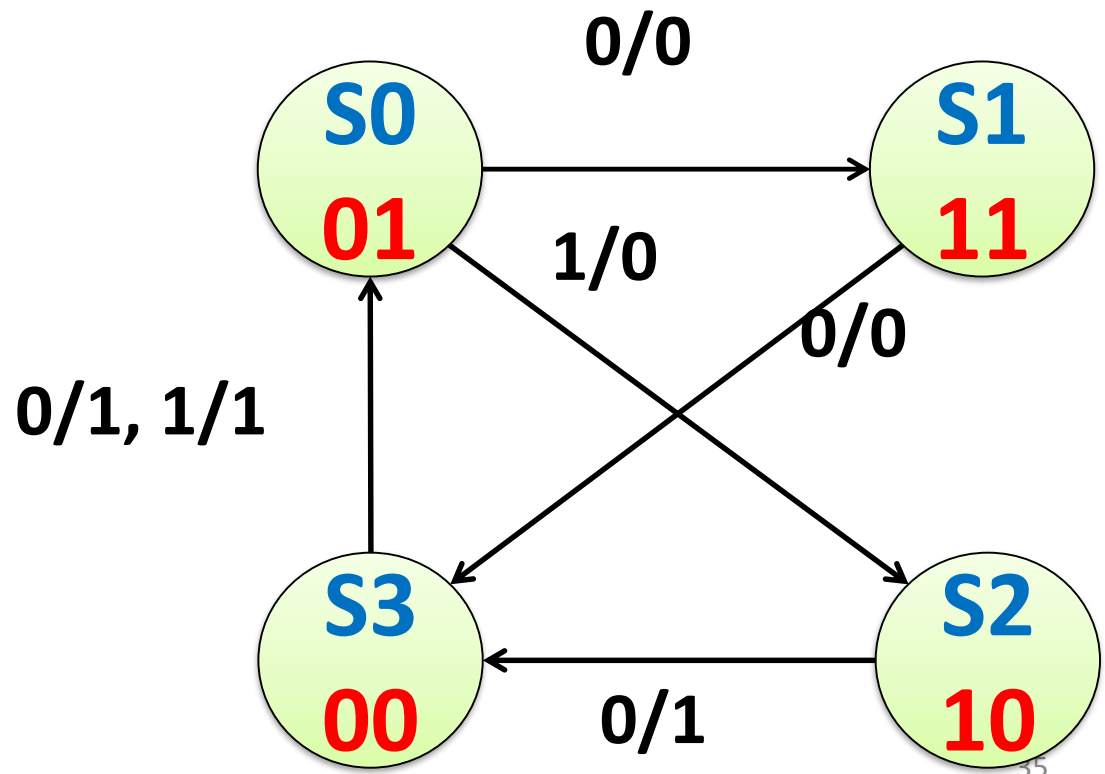
# Applying Rules 1,2 and 3

- Rule 1:  $S1, S2 \implies HD(11, 10)=1$
- Rule 2 :  $S1, S2$
- Rule 3:  $S0, S1$  and  $S2, S3$ 
  - $HD(S0,S1)=1$
  - $HD(S2,S3)=1$
- $HD(S0,S2)=2$
- $HD(S1,S3)=2$



# Example of State Assignment

Present state	Next state, output (Z)	
	Input, X	
	0	1
A	C, 0	D, 0
B	C, 0	A, 0
C	B, 0	D, 0
D	A, 1	B, 1

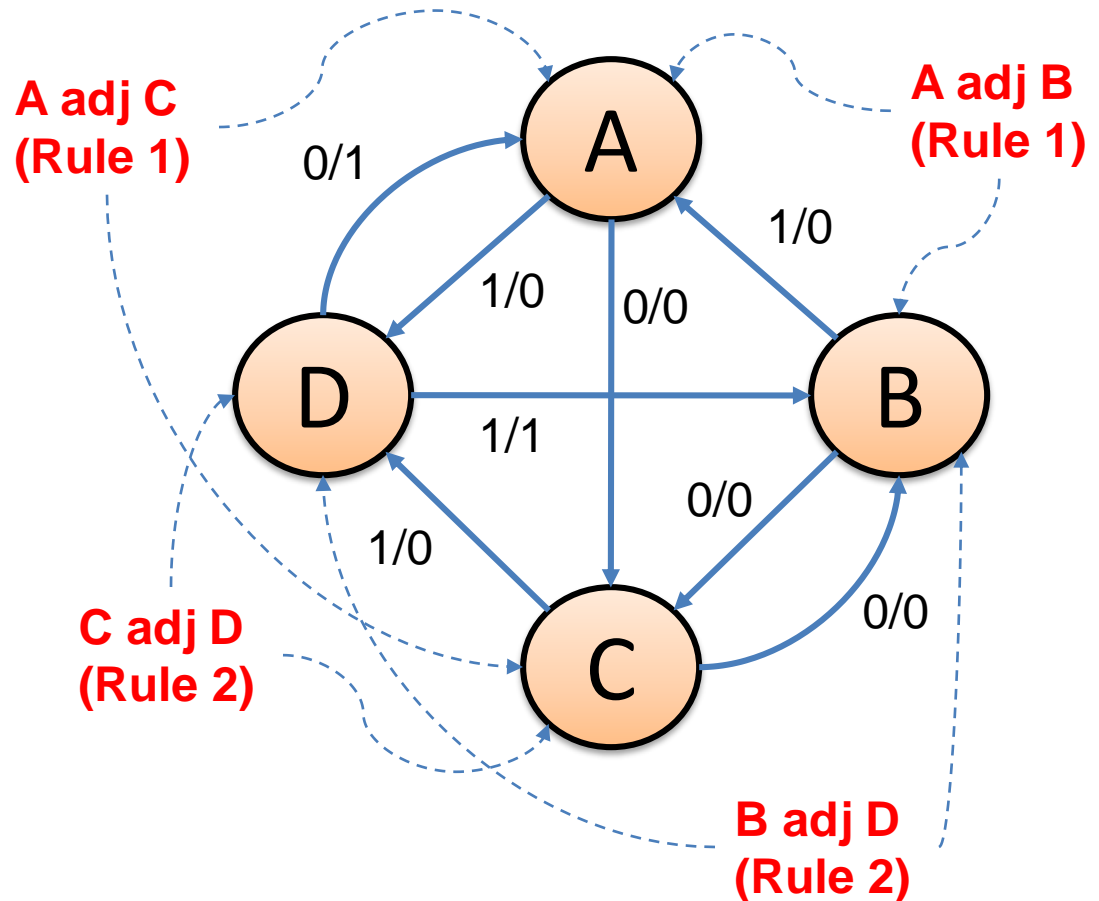


Rule 1: A and C goes to same next state D for same input 1

Rule 1: A and B goes to same next state C for same input 0

# Example of State Assignment

Present state	Next state, output (Z)	
	Input, X	
	0	1
A	C, 0	D, 0
B	C, 0	A, 0
C	B, 0	D, 0
D	A, 1	B, 1

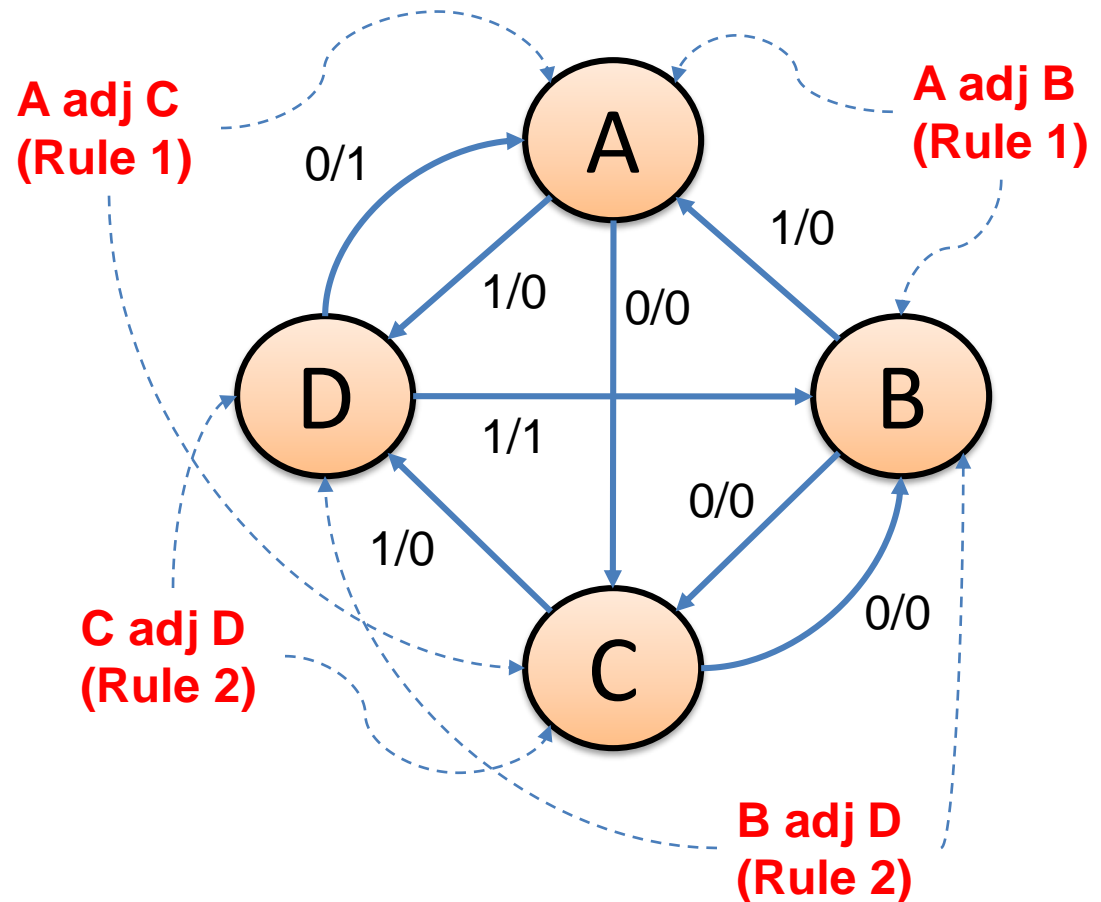


Rule 2: C and D are next state of A for input 0 and 1

Rule 2: B and D are next state of C for input 0 and 1

# Example of State Assignment


Present state	Next state, output (Z)	
	Input, X	
	0	1
A	C, 0	D, 0
B	C, 0	A, 0
C	B, 0	D, 0
D	A, 1	B, 1

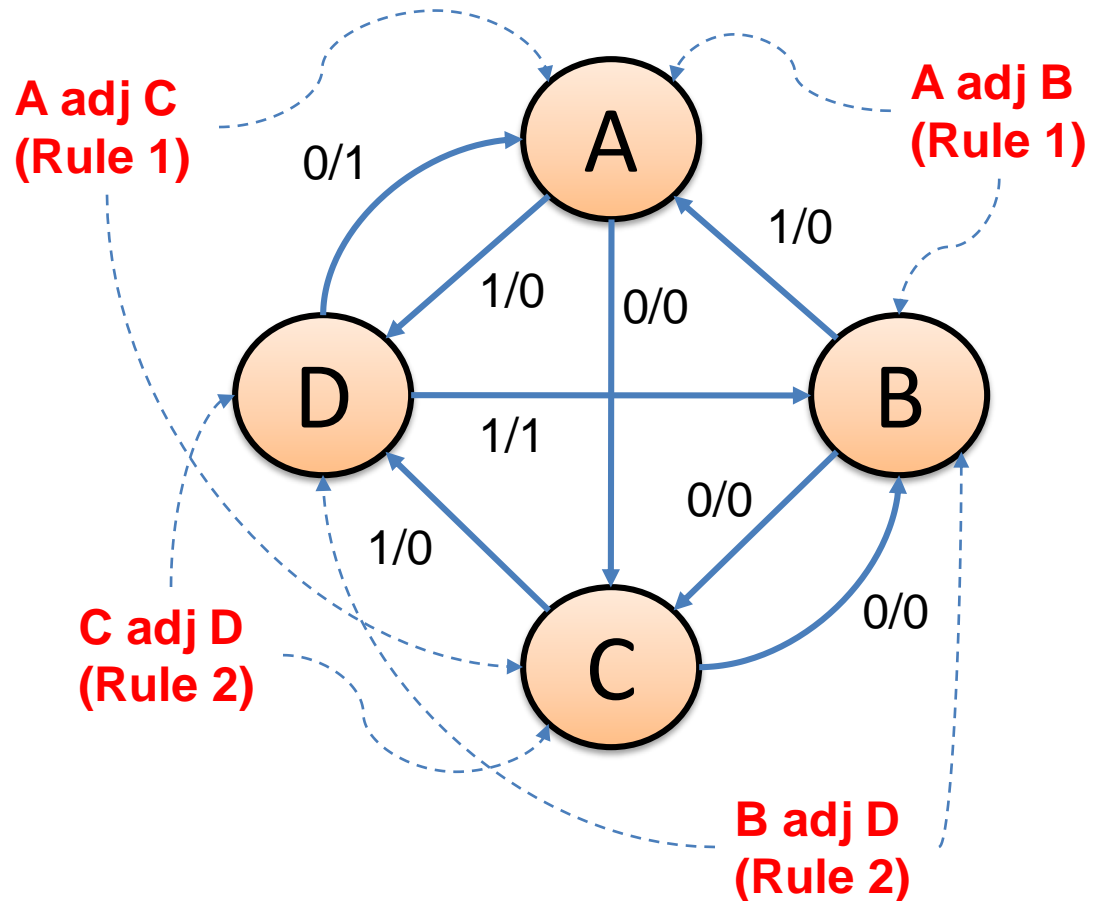

# Example of State Assignment

Present state	Next state, output (Z)	
	Input, X	
	0	1
A	C, 0	D, 0
B	C, 0	A, 0
C	B, 0	D, 0
D	A, 1	B, 1

	0	1
0	A	B
1	C	D

 

*Verify that BC and AD are not adjacent.*

# State Assignment #1


**A = 00, B = 01, C = 10, D = 11**

Present state	Next state, output Y1*Y2*, Z	
Y1, Y2	Input, X	
	0	1
A = 00	10 / 0	11 / 0
B = 01	10 / 0	00 / 0
C = 10	01 / 0	11 / 0
D = 11	00 / 1	01 / 1

Input	Present state		Output	Next state	
X	Y1	Y2	Z	Y1*	Y2*
0	0	0	0	1	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	0	0	0
1	1	0	0	1	1
1	1	1	1	1	0


 
# Logic Minimization for Optimum State Assignment



## Using an Arbitrary State Assignment:

A = 00, B = 01, C = 11, D = 10

Present state	Next state, output	
	Y1*Y2*, Z	
	Input, X	
Y1, Y2	0	1
A = 00	11 / 0	10 / 0
B = 01	11 / 0	00 / 0
C = 11	01 / 0	10 / 0
D = 10	00 / 1	01 / 1

Input	Present state		Output	Next state	
	Y1	Y2		Y1*	Y2*
X			Z		
0	0	0	0	1	1
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	1	0	1
1	1	1	0	1	0

# Logic Minimization for Arbitrary State Assignment

