

CS221: Digital Design

ASM/ FSMD/ RTL Design

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

Outline

- Drawbacks of state diagrams for real systems
- FSMD/ASM
- ASM Specification
- Comparison of FSM Vs ASM
 - Conversion of FSM to ASM, vice versa
- RTL Design

Reference Material for Lec 33, 34, 35

- Chapter 8 of Mano Book
 - Design at Register Transfer Level
 - Classic Example: Booth Multiplication
- Chapter 15 of Kumar Book
 - Algorithmic State Machine

Algorithmic State Machine

Algorithmic State Machine –

- Another representation of a Finite State Machine
- Suitable for FSMs with
 - a larger number of inputs and outputs
- As compared to FSMs expressed using
 - state diagrams and
 - state tables.


ASM Overview

- We need to separate controller & data processor
 - Controller – What actions need to be taken?
What is fundamental operating mode?
 - Processor – Undertake the action.
Manipulate the data

**The ultimate Goal of this course : Design
using Control Path + Data Approach : RTL
Design**

ASM Overview

- Control and data path interaction

 


- Our circuit is now explicitly separated


ASM Design : ASM Chart

- ASM charts are like flowcharts, with a few crucial differences.
- Be careful, especially with timing.
- Three type components/Box
 - **State Box**
 - **Decision Box**
 - **Combinational Box/Transition Box/Conditional Box**


ASM charts : 3 Elements used

 

(a) State box

 


(b) Decision box

 

(c) Conditional output box

ASM Design : State Box

- State Box – one box per system state

 


ASM Design : State Box

- Operation notation:
 - Sum \leftarrow 0 or Carry \leftarrow 0 or LOAD A
 - Combinational variable: $S=0$, $T=S+V$
- Idea: keep operations abstract & high level.
 - Don't work in detailed language of processing logic (i.e. write Sum \leftarrow 0, not $\text{CLR}_{\text{Sum Reg}}=1$)
- Operations will take place at the end of the clock period

ASM: State Box

 
- **State box** – represents a state.
- Equivalent to a node in a state diagram or a row in a state table.
- Contains **register transfer** actions or output signals
- **Moore-type outputs are listed inside of the box.**



ASM: State Box

- It is customary to write only the name of the signal that has to be asserted in the given state,
 - e.g., `z` instead of `z<=1`.
- Also, it might be useful to write an action to be taken,
 - e.g., `count <= count + 1`,
- And only later translate it to asserting a control signal that causes a given action to take place
 - (e.g., enable signal of a counter).

State name

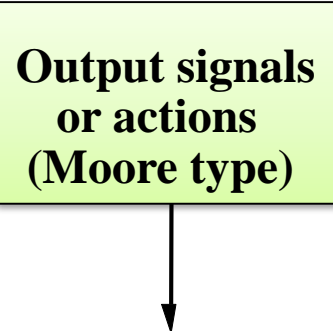


The diagram shows a light green rectangular box with a black border. Inside the box, the text "Output signals or actions (Moore type)" is written in bold black font. An arrow points from the text "State name" above to the top of the box. Another arrow points from the bottom of the box downwards.

**Output signals
or actions
(Moore type)**

ASM Design : Decision Box

 - Decision Box - Basic condition, i.e. logic flow control.
- Only the decision boxes depend on inputs.




ASM Design : Decision Box

- **Decision box** – indicates that
 - a given condition is to be tested and
 - the exit path is to be chosen accordingly
- The condition expression may include
 - One or more inputs to the FSM.

Vector Decision Box

 - A hexagon with:
 - One Input Path (entry point).
 - A vector of input conditions, placed in the center of the box, that is tested.
 - Up to 2^n output paths. The path taken has a binary vector value that matches the vector input condition




ASM Design

- Keep conditions as general as possible.
- Prefer: Carry high? Over $Q_{FF\#5}=1$?

ASM Design: Conditional Box

 - Conditional Box - An action/operation
 - to be undertaken conditioned on some earlier decision box.




ASM Design Vs Flowchart

- Conditional boxes do not appear in normal flowcharts.
- The essential difference is timing:
 - Flowcharts are sequential
 - ASM charts are not. All of the operations associated with a given state take place simultaneously.

ASM Design: Conditional Output Box

 
- **Conditional output box**
- Denotes output signals that are of the Mealy type.
- The condition that determines whether such outputs are generated is specified in the decision box.




ASMs representing simple FSMs

- Algorithmic state machines can model both
 - Mealy FSM
 - Moore Finite State Machines
- **They can also model machines that are of the mixed type**

Example 1: Draw ASM of D-FF

 


FSM

 


ASM

Example 2: Draw ASM of JK-FF

 


FSM

 

ASM

 
Moore FSM – Example 3: Sequence of two 1's




Moore FSM – Example 3: Sequence of two 1's

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Example 3: ASM Chart for Moore FSM

 


FSM


 


ASM

 
Mealy FSM –Example 4: Sequence of two 1's




ASM Chart for Mealy FSM – Example 4

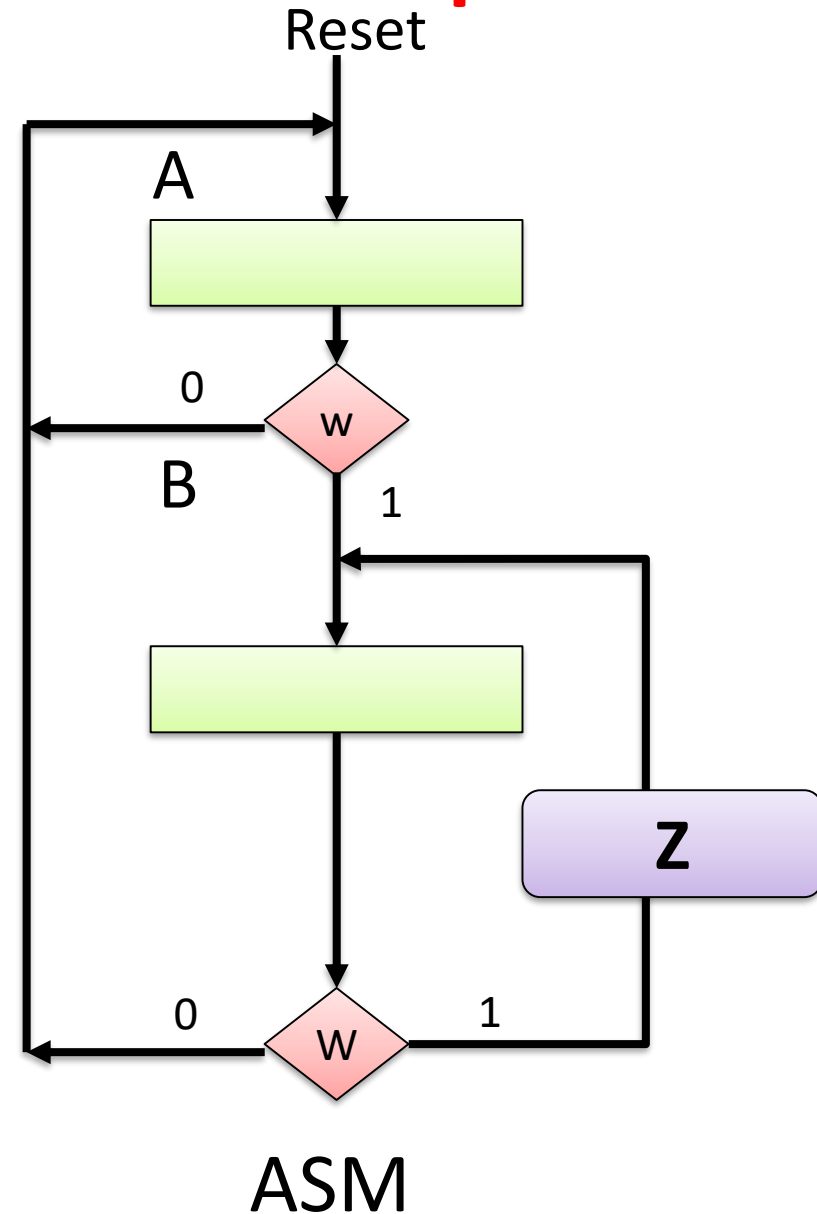 

ASM Chart : Example 5, mod 5 counter

 


FSM

 

ASM

ASM Chart : Example 6: 10 bit counter


FSM not
possible to
Draw/Tabulate

 


Require : addition, comparison data path
In state : We can put RTL like statement
 $C=C+1, X=COMPARE(C, 1023)$

Remember : Serial Addition

- Model S in terms of X, Y and Q (State)

 


Mealy FSM for Binary Adder

 


FSM


Mealy FSM for Binary Adder

 

FSM

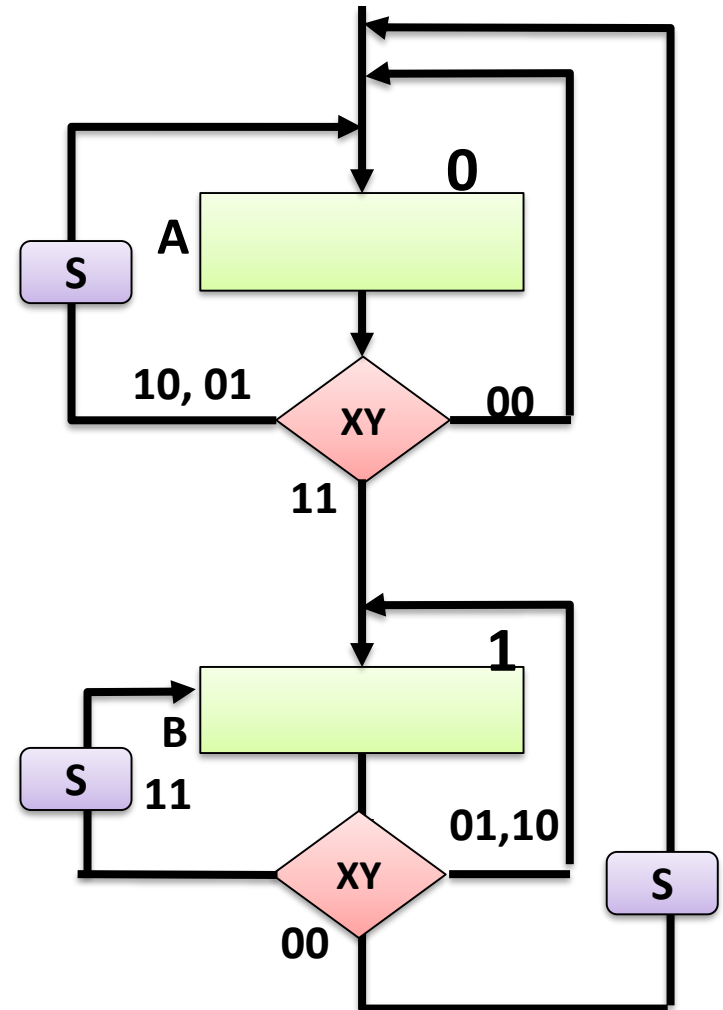


Mealy FSM for Binary Adder

 

FSM


ASM
Blocks

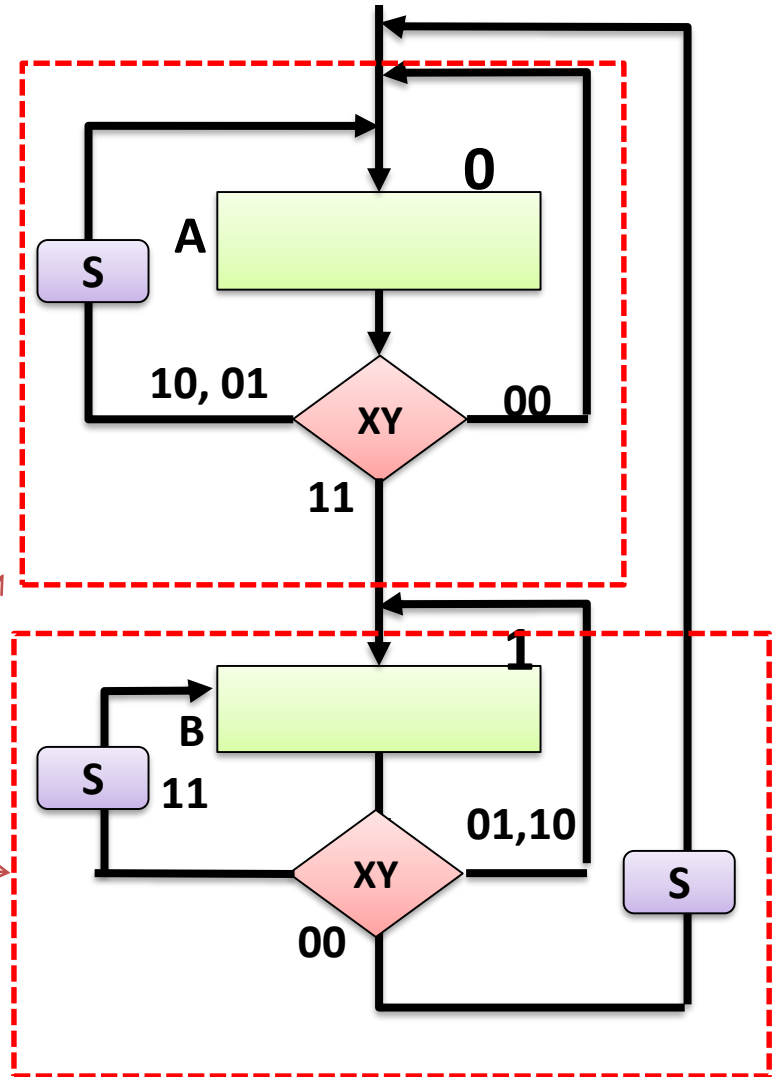


Mealy FSM for Binary Adder

- ASM Blocks
 - Two blocks in this example
- An ASM Block
 - Include a state and all its outgoing edges, condition boxes and conditional state boxes
 - All the parts of an ASM block execute in one cycle

ASM
Blocks

 

Mealy FSM for Binary Adder

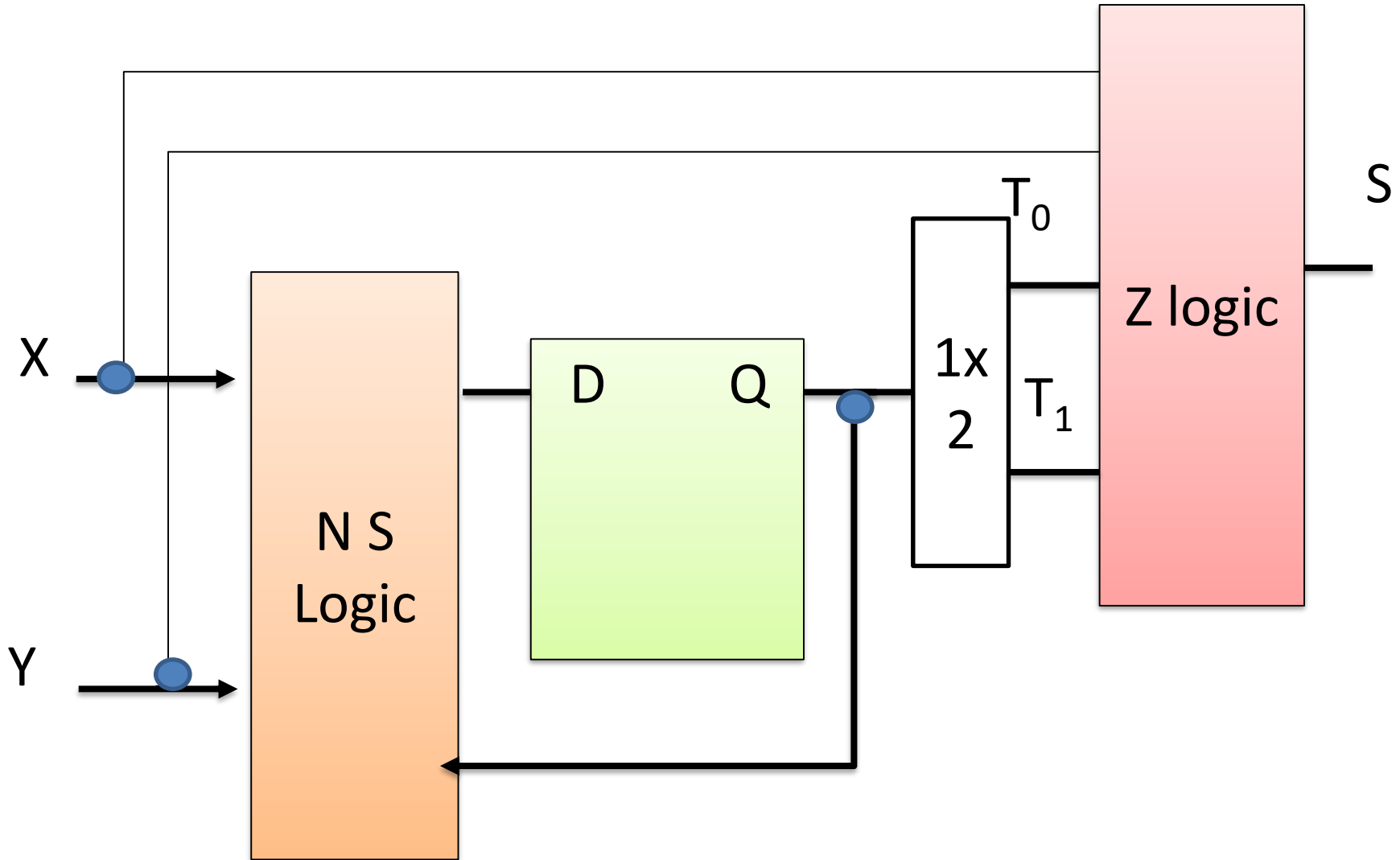

Mealy FSM for Binary Adder

