

CS221: Digital Design

RTL Design: Serial Multiplier

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

Outline

- RTL Design
- Modulo 14 Counter Example
- Serial Multiplier Example
- **Can we automate this RTL design process?**
 - **Given C code/Parallel Code**

Reference Material for Lec 33, 34, 35

- Chapter 8 of Mano Book
 - Design at Register Transfer Level
 - Classic Example: Serial Binary Multiplication
- Chapter 15 of Kumar Book
 - Section 15.5.1: Data path Subsystem for Binary Multiplier

ASM Charts: An Complete Example

Ref: Mano Book

ASM Charts: An Example


Mod 14 counter:

- There is a 4 bit counter (A)
- E specify: less than 12 or less than 4
- EF=11 specify : value =12,
 - It time to reset after next counting
- E depends of A_2 , F depends on A_2, A_3

If $A_2=1 \rightarrow E=1$, else $E=0$

$A_3A_2=1, \rightarrow F=1$, counter reset

AMS DP+CP : to be High Level

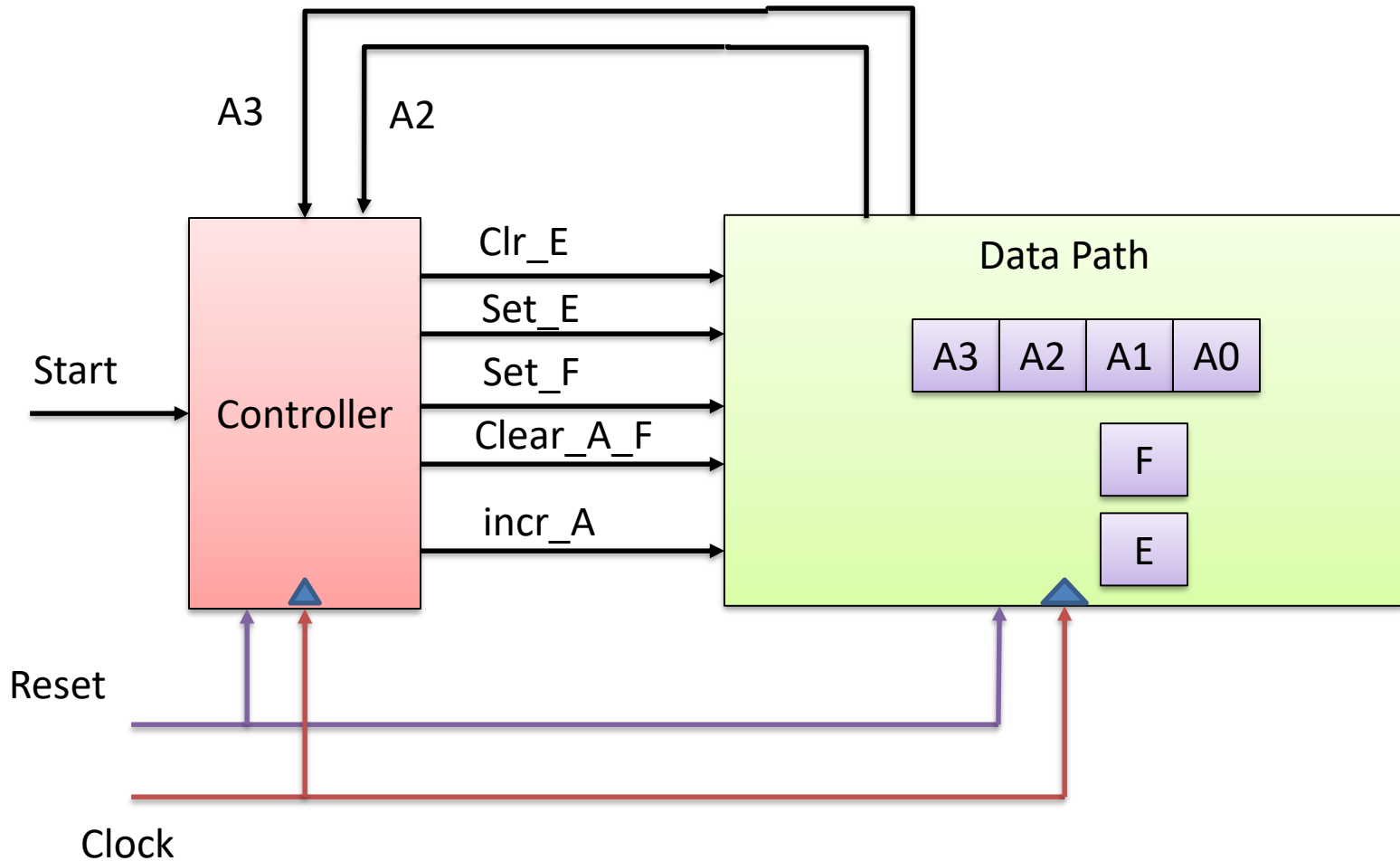


ASM Charts: An Example

- A is a register;
- A_i stands for i^{th} bit of the A register.

$$A = A_3A_2A_1A_0$$


- E and F are single-bit flip-flops.

 

Timing in ASM Charts

- Operations of ASM can be illustrated through a timing diagram.
- Two factors which must be considered are
 - Operations in an **ASM block** occur at the same time in ***one clock cycle***
 - Decision boxes are dependent on the status of the ***previous clock cycle*** (that is, they do not depend on operations of current block)

Timing in ASM Charts

 


Timing in ASM Charts

- Operations of ASM can be illustrated through a timing diagram.
- Two factors which must be considered are
 - Operations in an ASM block occur at the same time in *one clock cycle*
 - Decision boxes are dependent on the status of the *previous clock cycle* (that is, they do not depend on operations of current block)

Timing in ASM Charts

CTR	E, F	Conditions	State
0000	1,0	$A_2=0, A_3=0$	T1
0001	0,0	--	--
0010	0,0	---	--
0011	0,0	---	--
0100	0,0	$A_2=1, A_3=0$	--
0101	1,0	--	--
0110	1,0	--	--
0111	1,0	--	--
1000	1,0	$A_2=0, A_3=1$	--
1001	0,0	--	--
1010	0,0	--	--
1011	0,0	--	--
1100	0,0	$A_2=1, A_3=1$	--
1101	1,0		T2
1101	1,1		T0

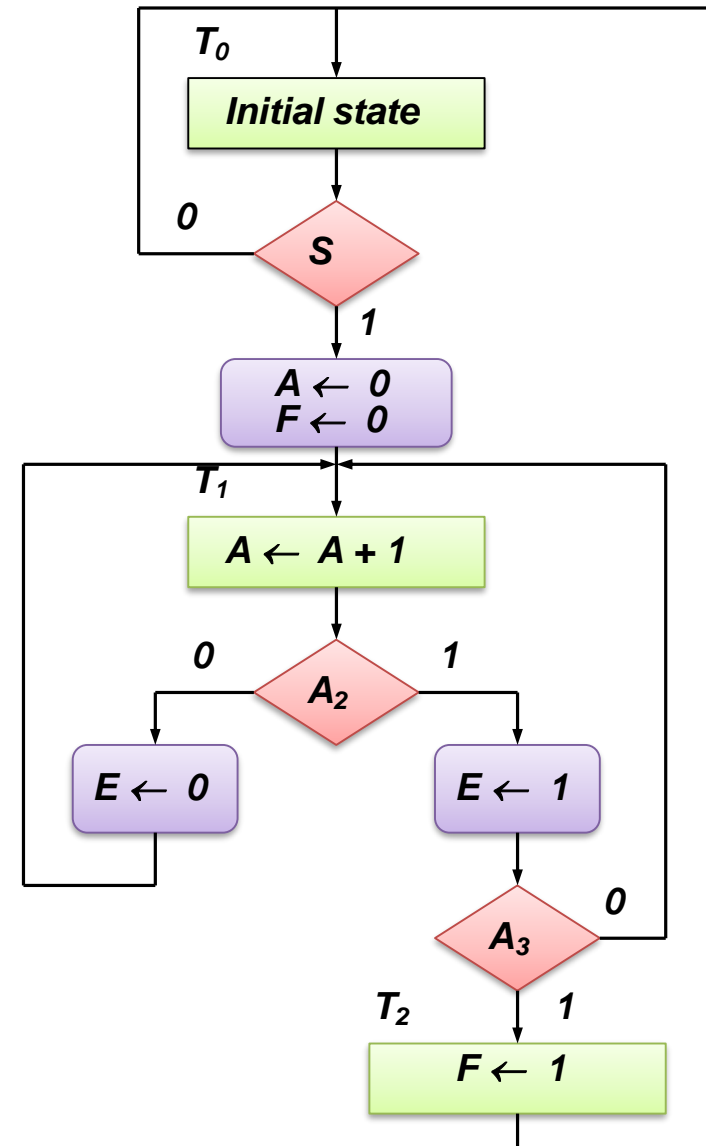



ASM Chart => Digital System

- ASM chart describes a digital system. From ASM chart, we may obtain:
 - Controller logic (via State Table/Diagram)
 - Architecture/Data Processor
- Design of controller is determined from the decision boxes and the required state transitions.
- Design requirements of data processor can be obtained from the operations specified with the state and conditional boxes.

ASM Chart => Controller

- Procedure:
 - Step 1: Identify all states and assign suitable codes.
 - Step 2: Formulate state table using
 - State** from state boxes
 - Inputs** from decision boxes
 - Outputs** from operations of state/conditional boxes.
 - Step 3: Obtain state/output equations and draw circuit.

ASM Chart => Controller

  

Assign codes to states:

$T_0 = 00$

$T_1 = 01$

$T_2 = 11$

Present state		inputs			Next state		outputs		
G_1	G_0	S	A_2	A_3	G_1^+	G_0^+	T_0	T_1	T_2
0	0	0	X	X	0	0	1	0	0
0	0	1	X	X	0	1	1	0	0
0	1	X	0	X	0	1	0	1	0
0	1	X	1	0	0	1	0	1	0
0	1	X	1	1	1	1	0	1	0
1	1	X	X	X	0	0	0	0	1

Inputs from conditions in decision boxes.

Outputs = present state of controller.

ASM Chart => Architecture/Data Processor


- Architecture is more difficult to design than controller.
- Nevertheless, it can be deduced from the ASM chart. In particular, the operations from the ASM chart determine:
 - What registers to use
 - How they can be connected
 - What operations to support
 - How these operations are activated.
- Guidelines:
 - always use high-level units
 - simplest architecture possible.

ASM Chart => Architecture/Data Processor

- Various operations are:
 - Counter incremented ($A \leftarrow A + 1$) when state = T_1 .
 - Counter cleared ($A \leftarrow 0$) when state = T_0 and $S = 1$.
 - E is set ($E \leftarrow 1$) when state = T_1 and $A_2 = 1$.
 - E is cleared ($E \leftarrow 0$) when state = T_1 and $A_2 = 0$.
 - F is set ($F \leftarrow 0$) when state = T_2 .
 - F is cleared ($F \leftarrow 0$) when state = T_0 and $S = 1$.
- Deduce:
 - One 4-bit register A (e.g.: 4-bit synchronous counter with clear/increment).
 - Two flip-flops needed for E and F (e.g.: JK/D flip-flops).

Processor

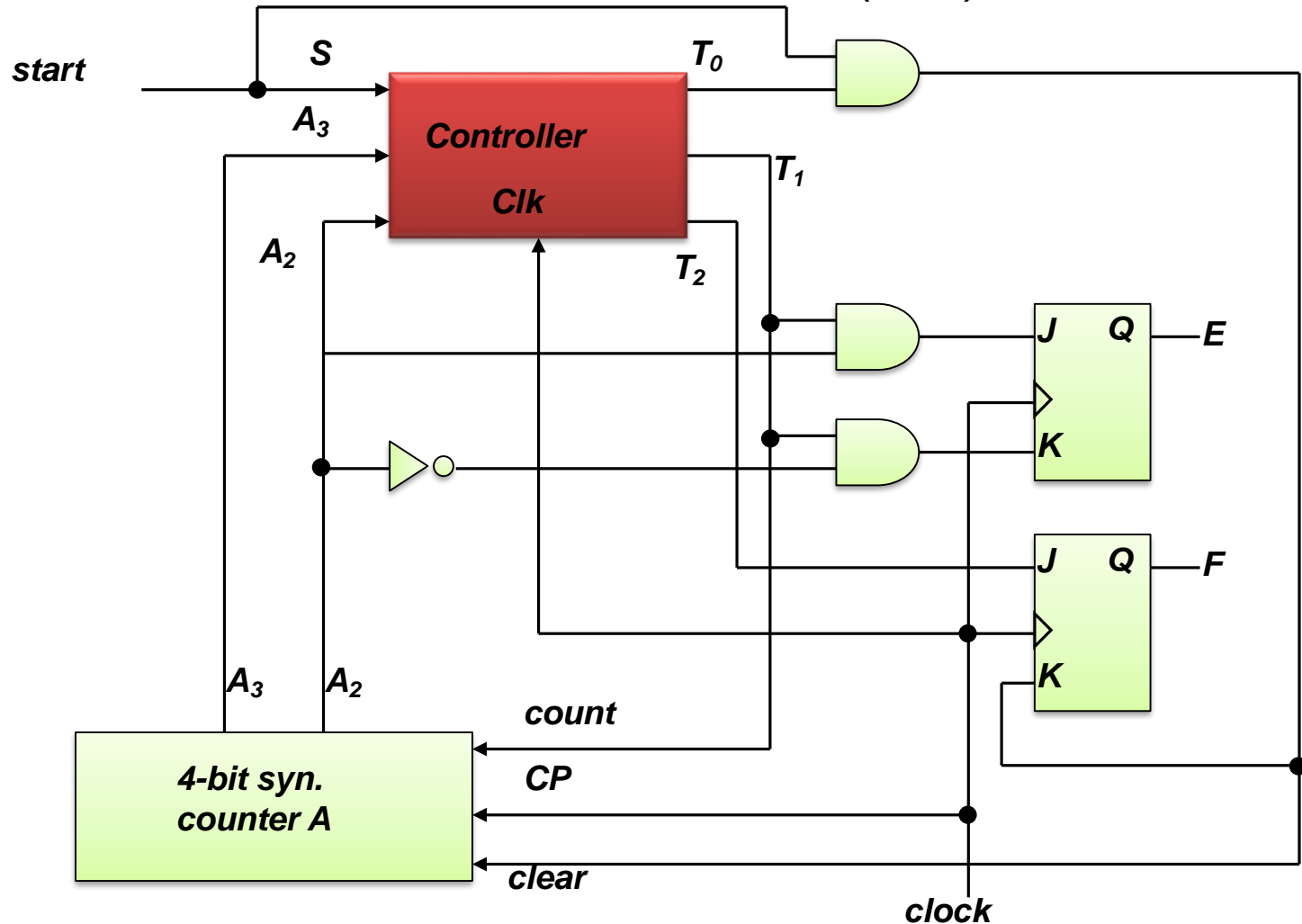$(A \leftarrow A + 1)$ when $state = T_1$.
 $(A \leftarrow 0)$ when $state = T_0$ and $S = 1$.
 $(E \leftarrow 1)$ when $state = T_1$ and $A_2 = 1$.



RTL/ASM example
for
8 bit Sequential Multiplier

Ref: Mano Book

RTL: Multiplier Example

- Example: (101×011) Base 2
- Note that the partial product summation for n digits, base 2 numbers requires adding up to n digits (with carries) in a column.
- Note also $n \times m$ digit multiply generates up to an $m + n$ digit result (same as decimal).

■ Partial products are:

101×0 , 101×1 , and 101×1

$$\begin{array}{r}
 101 \\
 \times 011 \\
 \hline
 101 \\
 101 \\
 000 \\
 \hline
 001111
 \end{array}$$

Example (1 0 1) x (0 1 1) Again


- Reorganizing example to follow hardware algorithm:

		1	0	1				
	x	0	1	1				
→	0	0	0	0		Clear C A		
→	+	1	0	1		Multiplier0 = 1 => Add B		
→	0	1	0	1		Addition		
→	0	0	1	0	1	Shift Right (Zero-fill C)		
→	+	1	0	1		Multiplier1 = 1 => Add B		
→	0	1	1	1	1	Addition		
→	0	0	1	1	1	1	Shift Right	
→	0	0	0	1	1	1	1	Multiplier2 = 0 => No Add, Shift Right

Binary Multiplication

- Polynomial Multiplication
 - You can think Binary number A, B as polynomials
 - $A(X) = A_{n-1} \cdot 2^{n-1} + \dots + A_2 \cdot 2^2 + A_1 \cdot 2^1 + A_0 \cdot 2^0$
 - Multiply polynomial to get another one
 - Time complexity: $O(n^2)$ Basic serial Algorithm, $O(n^{1.5})$ for divide conquer approach, $O(n \lg n)$ using FFT
- Booth Algorithm reduce number Partial addition
 - 99 Represent using 100-1, 95 is 100-5
 - 111 represent as 1000-1 in binary: possibly reduce


Sequential Multiplier

 

Control Algorithm:

1. $P \leftarrow 0$, $A \leftarrow$ multiplicand, $B \leftarrow$ multiplier **//Initialization**
2. If LSB of $B == 1$ then add A to P else add 0
3. Shift $[P][B]$ right 1
4. Repeat steps 2 and 3 $n-1$ times.
5. $[P][B]$ has product.

Multiplier Example: Block Diagram

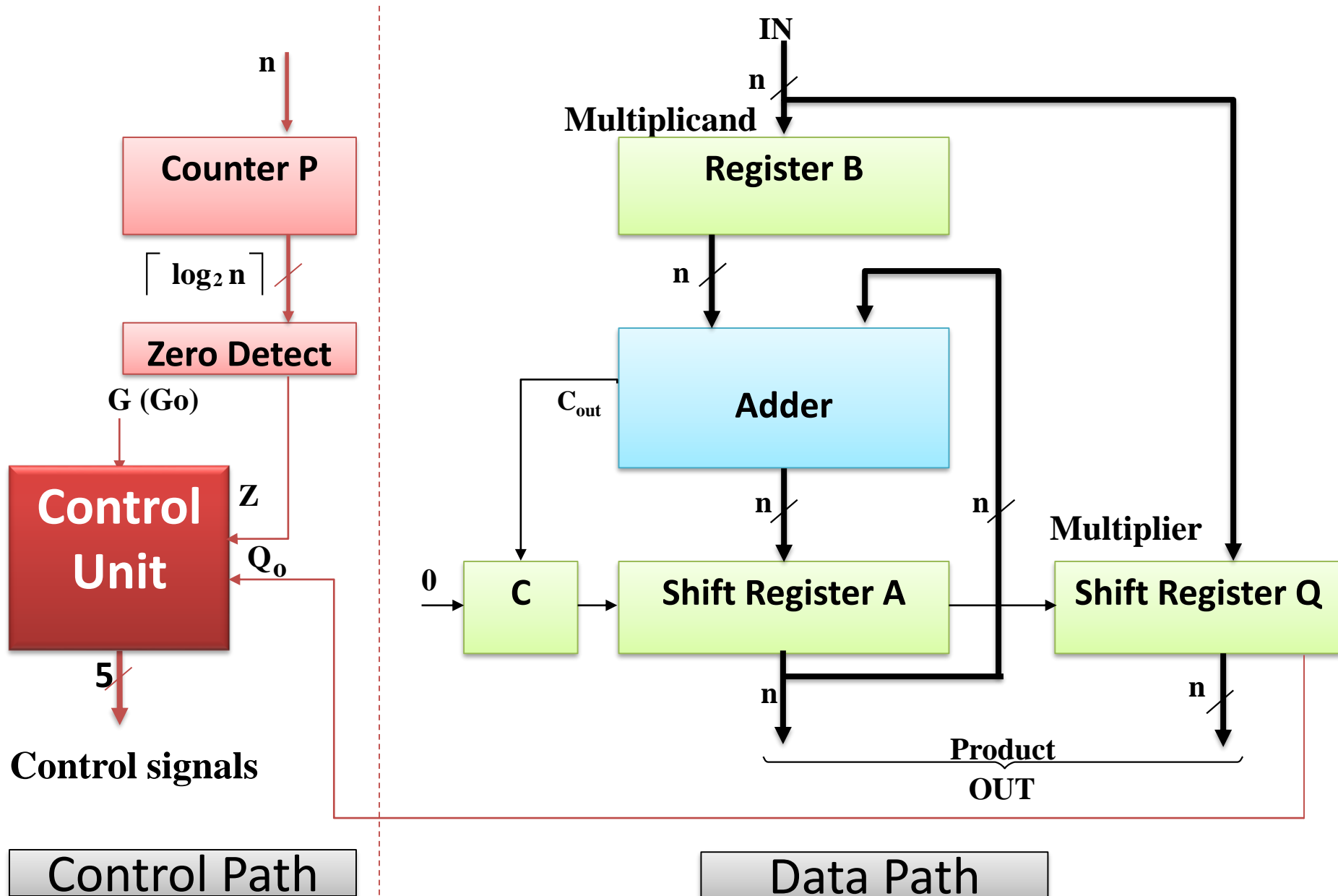


Multiplier Example: Operation

- Step1: The multiplicand (top operand) is loaded into register B.
- Step2: The multiplier (bottom operand) is loaded into register Q.
- Step3: Register C || A is initialized to 0 when G becomes 1.
- Step4: The partial products are summed iteratively in register C || A || Q.

Multiplier Example: Operation

- Step5: Each multiplier bit, beginning with the LSB, is processed (if bit is 1, use adder to add B to partial product; if bit is 0, do nothing)
- Step6: $C || A || Q$ is shifted right using the shift register
 - Partial product bits fill vacant locations in Q as multiplier is shifted out
 - If overflow during addition, the outgoing carry is recovered from C during the right shift
- Step 7: Steps 5 and 6 are repeated until Counter P = 0 as detected by Zero detect.
 - Counter P is initialized in step 4 to $n - 1$, n = number of bits in multiplier

Multiplier Example: ASM Chart

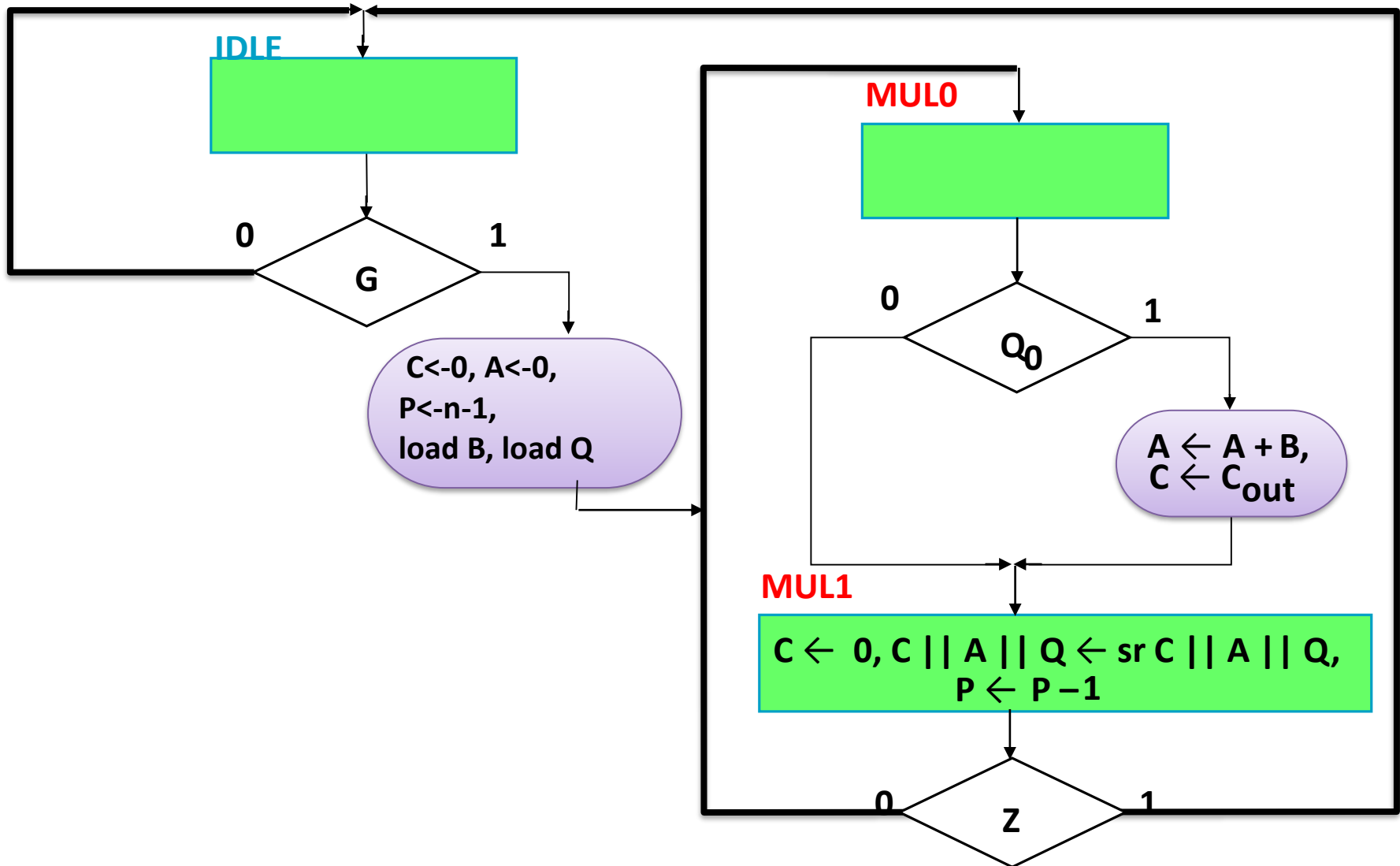

Multiplier Example: ASM Chart (continued)

- Combined Mealy - Moore output model
- **IDLE - state**
 - Input G is used as the condition for starting the multiplication, and
 - *C, A, and P are initialized and Load B, Load Q*
- **MUL0 - state**
 - Conditional addition is performed based on the value of Q_0 .
- **MUL1 - state**
 - Right shift is performed to capture the partial product and position the next bit of the multiplier in Q_0
 - the terminal count of 0 for down counter P is used to sense completion or continuation of the multiply.

Multiplier Example: Control Signal Table

Module	Micro Operations	Control Signal Name	Control Expression
Reg A	$A \leftarrow 0$ $A \leftarrow A + B$ $C A Q \leftarrow sr(C A Q)$	Load_regs Add_regs Shift CAQ	IDLE.G MUL0.Q ₀ MUL1
Reg B	$B \leftarrow IN$	Load_regs	LOAD_B
FF C	$C \leftarrow 0$ $C \leftarrow Cout$	Clear C Load	IDLE.G+MUL1 --
Reg Q	$Q \leftarrow IN$ $C A Q \leftarrow sr(C A Q)$	Load_regs ShiftCAQ	LOAD_Q
Ctr P	$P \leftarrow N-1$ $P \leftarrow P-1$	Load_regs Decr_P	MUL1

Multiplier Example: Control Circuit

PS	PS	Inputs			NS	Ready	Load Regs	Decr_ P	Add_ regs	Shift_ CAQ
		G	Q0	Z						
Idle	00	0	x	X	00	1				
Idle	00	1	X	x	01	1	1			
Mul0	01	x	0	X	10			1		
Mul0	01	x	1	X	10				1	
Mul1	10	x	x	0	01			1		1
Mul1	10	x	x	1	00			1		1

Ready=Idle


Load_Regs=Idle.G

Decr_P=Mul0

Add_regs=Mul0.Q₀

ShiftCAQ=Mul1

Multiplier Example: Control Circuit

 

$$N1 = D_1' D_0$$

$$N0 = D_1' D_0' G + D_1 D_0' Z'$$

$$\text{Ready} = \text{Idle}$$

$$\text{Load_Regs} = \text{Idle} \cdot G$$

$$\text{Decr_P} = \text{Mul1}$$

$$\text{Add_regs} = \text{Mul0} \cdot Q_0$$

$$\text{ShiftCAQ} = \text{Mul1}$$