

CS221: Digital Design

Sequential Logic Design

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

Post Midsem Topics

- **Part I : Basic Sequential Design**
 - Latch and Flip Flop : Design, Characteristics Eqn, excitation Table
 - Register, Multi-Function Register, Memory Design
 - Counter Design: Basic
- **Part II: Formal Sequential Design**
 - FSM Design : Spec, Implementation
 - FSM Optimization
- **Part III : Advanced Formal Sequential Design**
 - RTL: ASM Design, ASM implementation
 - Digital System Design using FPGA and HDL

Quizzes and Exam

- Will be in RapidFire Mode on MS Teams
- Two quizzes
 - Quiz 1 : Basic Sequential Design
 - Quiz 2 : Formal Sequential Design
- End Semester have three parts
 - Part I: Advanced Sequential Design
 - Part II: Basic and Formal Sequential Design
 - Part III: Pre-mid Semester part & Post mid sem part

Books to be referred

- **ManoBook:** M. Morris Mano and M. D. Ciletti, *Digital Design*, 4/e, Pearson Education India, 2007.
- **VahidBook:** Frank Vahid, *Digital Design (Preview Edition)*, Wiley India Edition, 2005 *[[FF and Register design]]*
- **KumarBook:** A. Anand Kumar, *Fundamentals of Digital Circuits* 3rd Edition, PHI. 2014 **((This book have a lot of examples to understand the concepts))** *[[ASM Chart]]*
- **KatzBook:** Randy H. Katz, G Borriello, *Contemporary Logic Design*, 2nd Edition, PHI, India, 2009 *[[FSM Opt.]]*
- **Givone Book:** Donald D. Givone, *Digital Principles and Design*, McGraw-Hill, 2003 *[[Counter Design]]*

Announcement


- There will be no CS221 class on 1st Oct and 3rd Oct ==> Coming Friday and Monday
- Both the Instructors will be out of town for JEE related work
- Makeup classes for 1st Oct and 3rd Oct are scheduled on 6th and 12th Oct at evening 5.30 to 6.30pm

Outline

- Combinational Vs Sequential Logic Design
- Design a **flip-flop**, that stores one bit
 - RS latch
- Stabilizing RS latch : Level Sensitive
- Clocked Latch : Flip Flop- Edge Sensitive
- D, JK, T flip flops
- Characterization Table and Equation
 - RS, D, JK and T Flip flop

Combinational Vs Sequential Logic

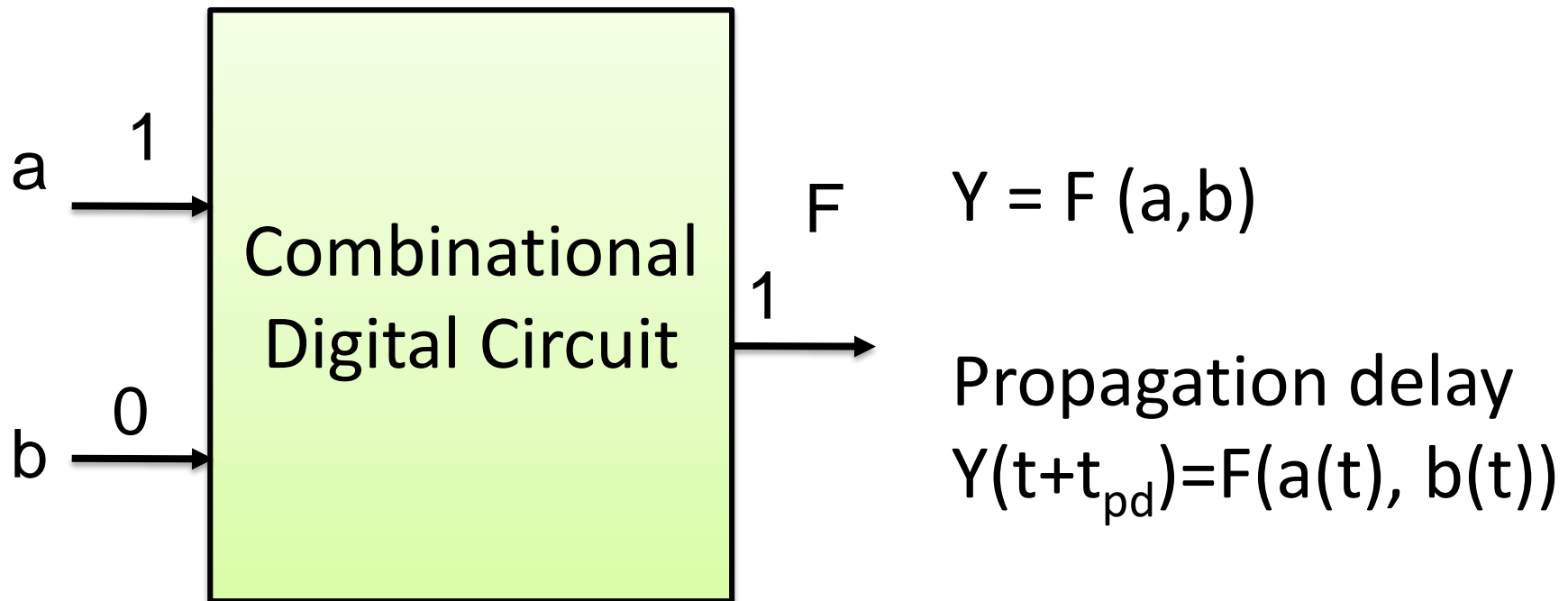- Combinational circuit
 - **Output depends on present input**
 - Examples: F (A,B,C), FA, HA, Multiplier, Decoder, Multiplexor, Adder, Priority Encoder




Combinational Vs Sequential Logic

- Sequential circuit
 - Output depends not just on present inputs
 - But also on past sequence of inputs (State)
 - Stores bits, also known as having “state”

Combinational Vs Sequential Logic

 - Simple example: a circuit that counts up in binary




Must know sequence of past inputs to know output

$$Y(t) = F(a(t), b(t), H)$$

H is History/Sequence/State

Sequential Circuit: Generic Circuit

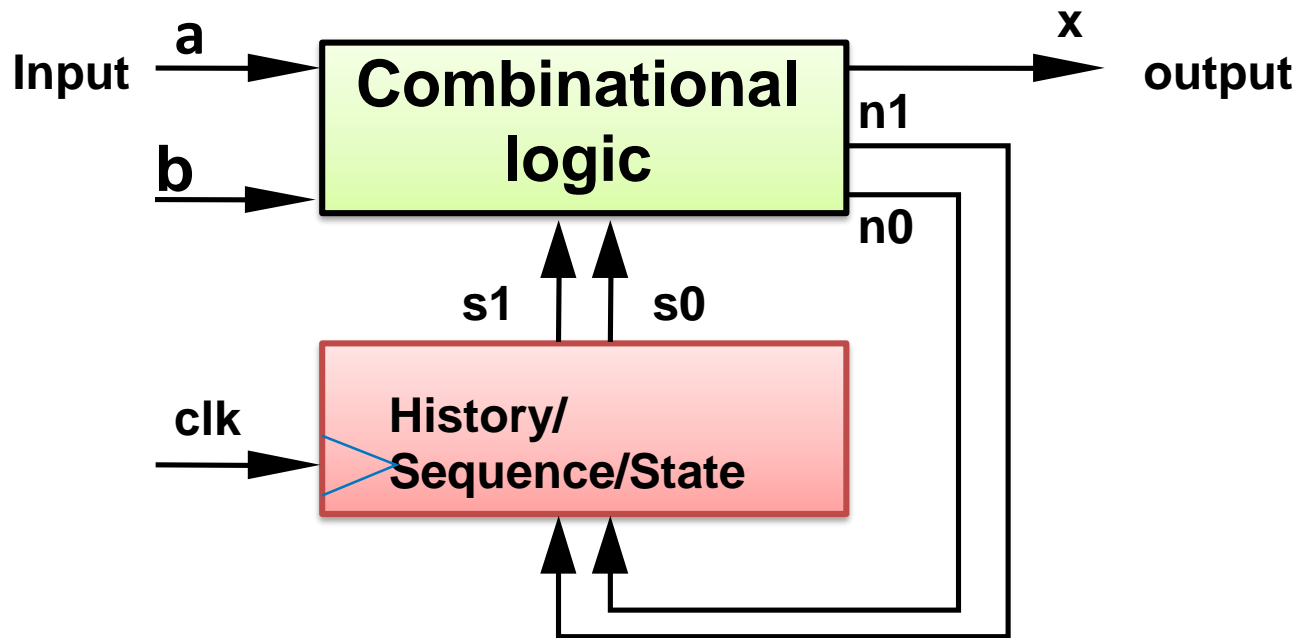

$$Y(t) = F(a(t), b(t), H)$$

H is History/Sequence/State

Where to
Store this
History

(Memory
Element)

Example Needing Bit Storage

- Mechanical Example: Retractable Ball point pen
 - Push to change : on or off
 - T-FFs




Example Needing Bit Storage

- Electronics Example: Flight attendant call button
 - Press call: light turns on
 - ***Stays on*** after button released
 - Press cancel: light turns off




How to design a circuit for this ?


Example Needing Bit Storage

 

1. Call button pressed – light turns on

 

2. Call button released – light stays on

 

3. Cancel button pressed – light turns off

Example Needing Bit Storage


- Flight attendant call button
 - Press call: light turns on
 - ***Stays on*** after button released
 - Press cancel: light turns off



How to design a
circuit for this ?

 Example Needing Bit Storage

- Flight attendant call button
 - Press call: light turns on : ***Stays on*** after button released
 - Press cancel: light turns off
- Logic gate circuit to implement this?




Doesn't work. $Q=1$ when $\text{Call}=1$, but doesn't stay 1 when Call returns to 0

Need some form of “feedback” in the circuit


First attempt at Bit Storage

 - We need some sort of feedback
 - Does circuit this circuit do what we want?



- No: Once **Q** becomes 1 (when **S**=1), **Q** stays 1 forever – no value of **S** can bring **Q** back to 0


First attempt at Bit Storage

 

Once Q becomes 1 (when $S=1$), Q stays 1 forever – no value of S can bring Q back to 0



Bit Storage Using an SR Latch

 - With cross-coupled NOR gates
 - Does the circuit to the right ?
 - Do what we want?




- Yes! How did someone come up with that circuit?
 - Maybe just trial and error, a bit of insight...

Bit Storage Using an SR Latch

  

Function Table of SR Latch


 


Set : make out put 1

Reset : make out put 0


S	R	Q	Q'	
1	0	1	0	
0	0	1	0	After S=1, R=0
0	1	0	1	
0	0	0	1	After S=0, R=1
1	1	0	0	Forbidden

Example Using SR Latch for Bit Storage

  

- SR latch can serve as bit storage of flight-attendant call button : 😊 😊 😊 Great
 - Call=1 : sets Q to 1
 - Q stays 1 even after Call=0
 - Cancel=1 : resets Q to 0
- **But, there's a problem...**

SR Latch with NAND Gates

 


S	R	Q+
0	0	1*0* (Unpredictable)
0	1	1
1	0	0
1	1	Q

Opposite to SR Latch with NOR Gates

Set will do $Q=0$ and Reset will $Q=1$

Problem with SR Latch: $SR=11$




 
- Problem
 - If $S=1$ and $R=1$ simultaneously, we don't know what value Q will take (Unpredictable)




Race Condition :-

**Who will win 0 or 1?
Eventually, what will be the
value of Q?**

Problem with SR Latch

    


 Q may oscillate. Then, because one path will be slightly longer than the other, Q will eventually settle to 1 or 0 – but we don't know which.



Solution to Race Condition

 - We try to avoid $S=1$ and $R=1$ by the following circuit



- Can we ensure value $S=1$ and $R=1$ will not happen at the same time?

Reference

VahidBook: Frank Vahid, Digital Design (Preview Edition), Wiley India Edition, 2005 [*FF and Register design*]

Thanks