

CS221: Digital Design

FPGA and HDL: Programmable Devices

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

Outline


- EDA : Can we automate Digital Design Process
- IC Design process, FPGA
- HDL Requirement of VHDL, Model
- IC and FPGA Based Design Process

Digital Design Automation


- Electronics Design Automation
 - Automation of Chip Design
 - Automation of Comb. Circuit Optimization
 - Automation of Sequential Circuit Generation : **Given a C like Statement of System: Ex- sum of 1st n odd number**
 - Generate ASM Automatically : Using Program
 - Infer Data Path and FSM/CP automatically: Using Program
 - Take Constraints: Size, Power, Components
- Simulation and Prototype: ModelSim, FPGA
- Specification Language: HDL

Serial Code Vs Parallel

 
- C Code: For ($i=0; i<8; i++$) $S = S + X[i];$
- In H/W



Design Flow: Hardware Vs Software

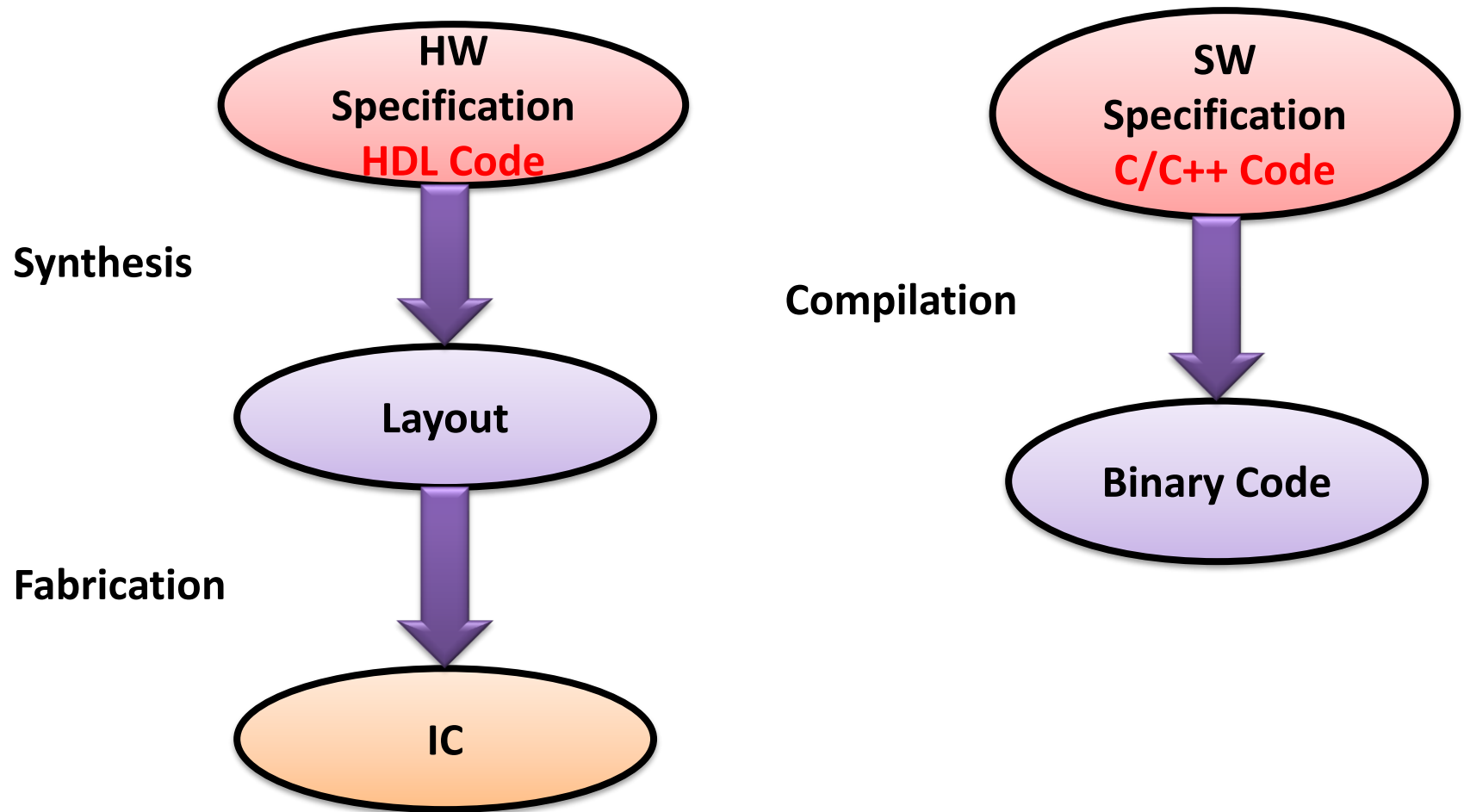

IC Design Process


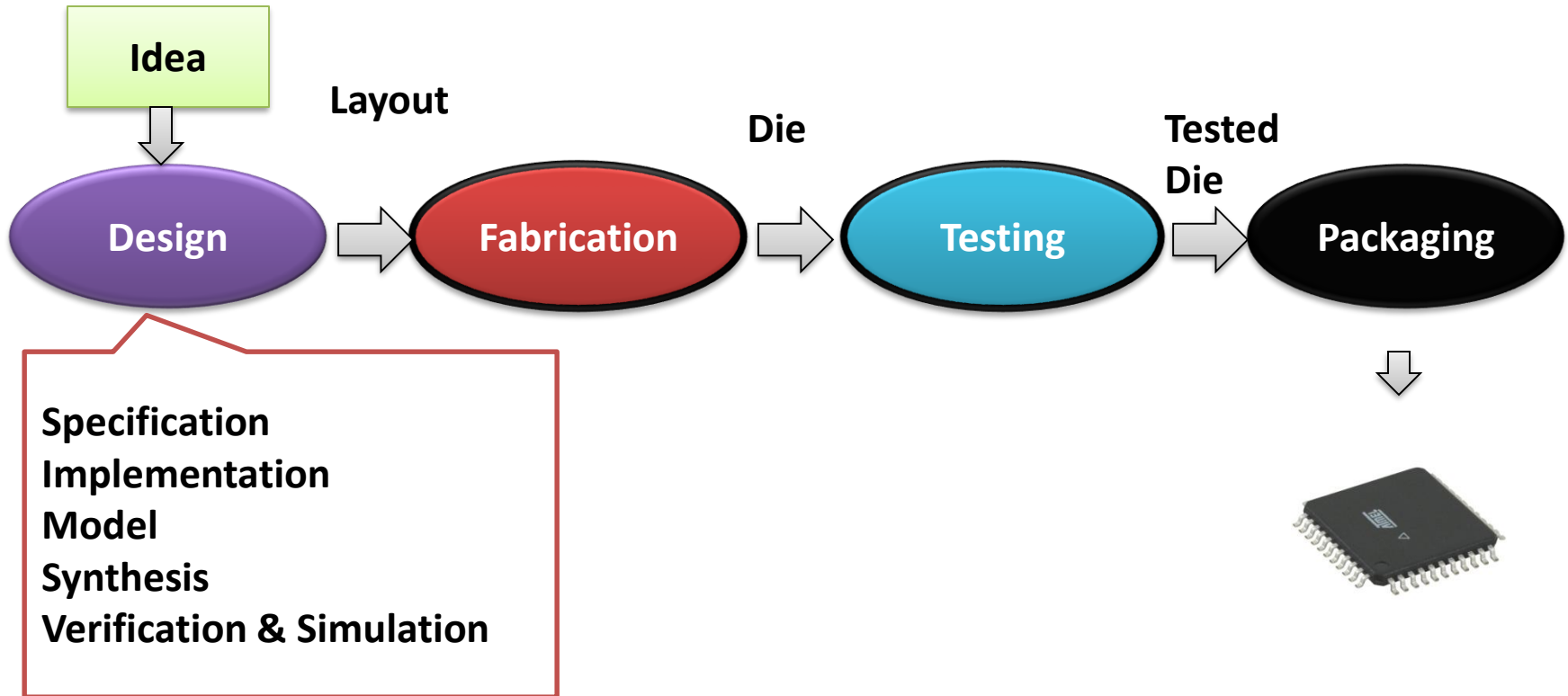


FPGA:-

Field Programmable Gate


Array

Multiplexor (Mux)

  

Covers All
Minterms


Implementing logic Function using MUX

 


Implementing 3 Inputs Logic Function using 4x1 MUX

$$F(A, B, C) = \sum m(1, 2, 6, 7)$$


A	B	C	F	F
0	0	0	0	C
0	0	1	1	
0	1	0	1	C'
0	1	1	0	
1	0	0	0	0
1	0	1	0	
1	1	0	1	1
1	1	1	1	

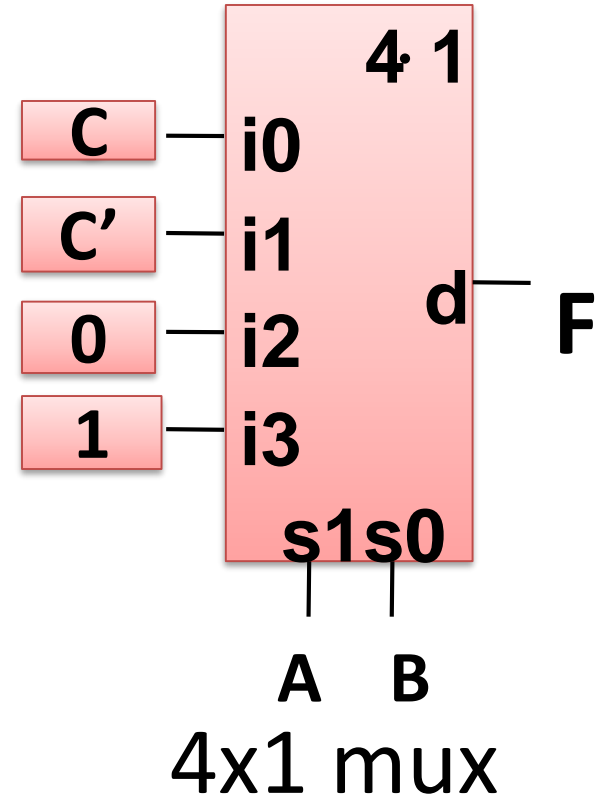

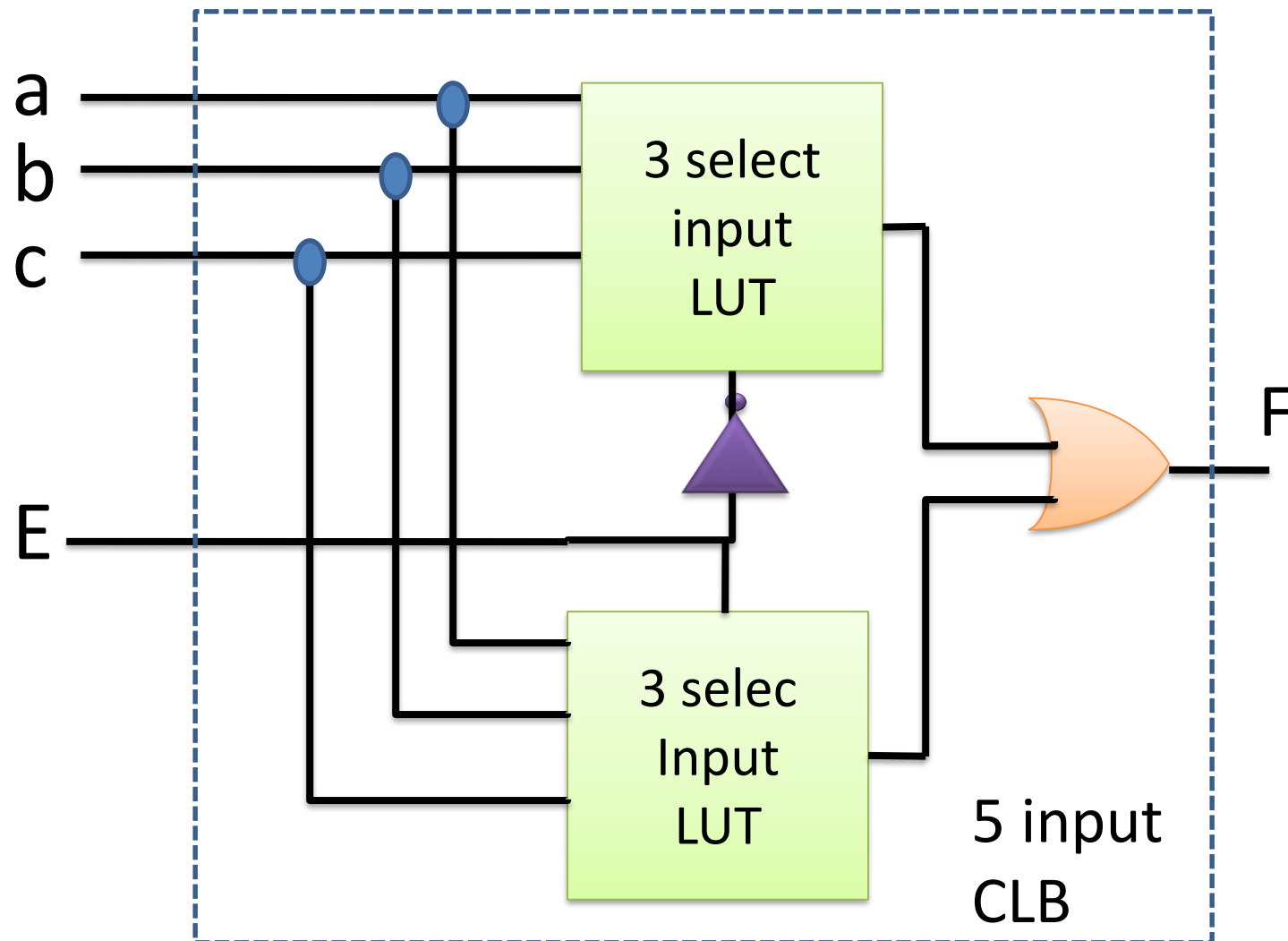Implementing 4 Inputs Logic Function using two 8x1 MUX



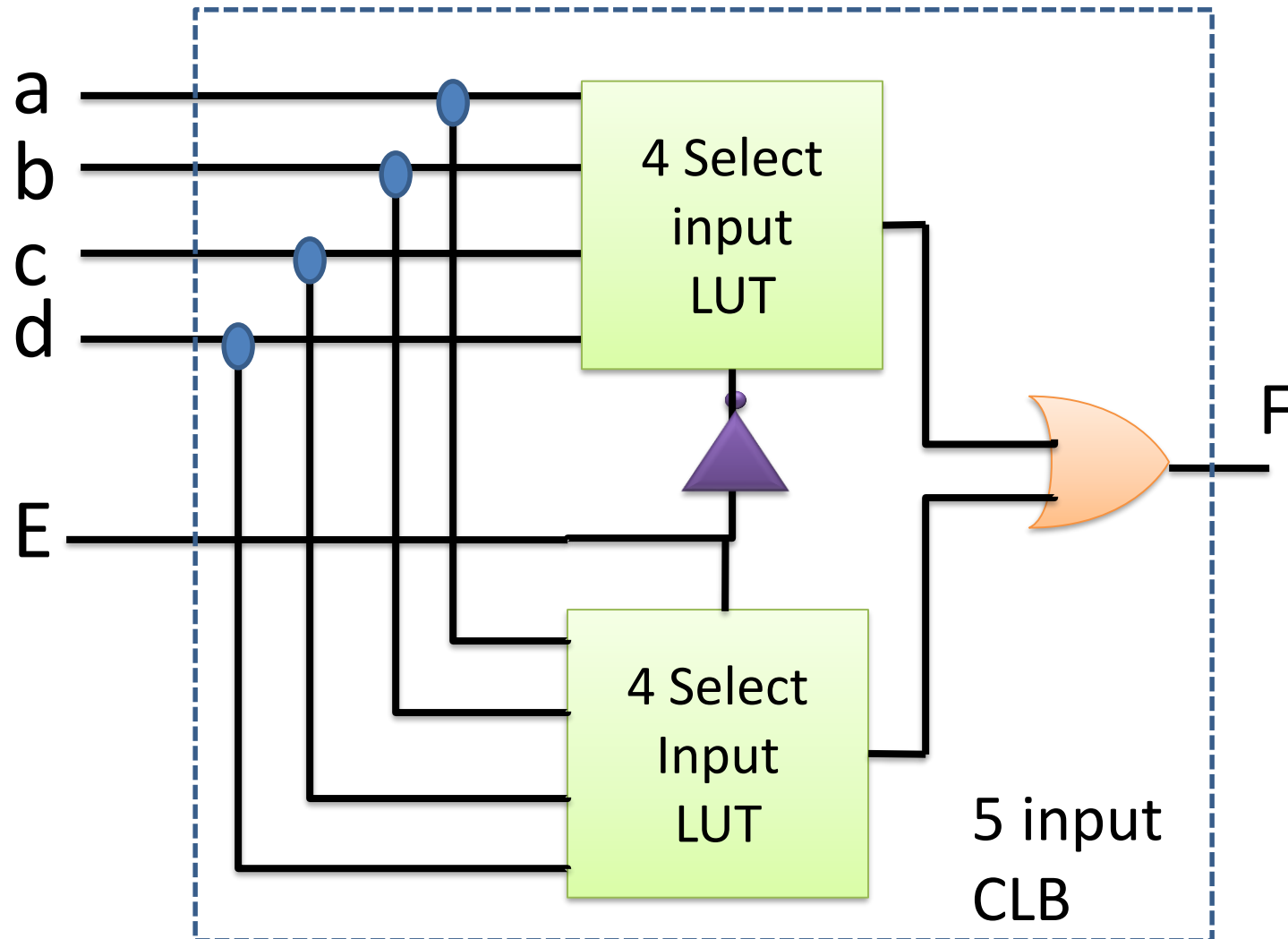Implementing 5 Inputs Logic Function using two 16x1 MUX



Shannon's expansion theorem

Used to implement many variable logic functions using MUX and LUTs

$$f(x_1, x_2, \dots, x_n) = x_1 f(0, x_2, \dots, x_n) + x_1 f(1, x_2, \dots, x_n)$$

Since x_1 is a boolean variable, we need to look at only two cases: $x_1 = 0$ and $x_1 = 1$.

- Setting $x_1 = 0$ in the above expression, we have:

$$\begin{aligned} \bullet f(0, x_2, \dots, x_n) &= 1 f(0, x_2, \dots, x_n) + 0 f(1, x_2, \dots, x_n) \\ &= f(0, x_2, \dots, x_n) \end{aligned}$$


- Setting $x_1 = 1$, we have:

$$\begin{aligned} \bullet f(1, x_2, \dots, x_n) &= 0 f(0, x_2, \dots, x_n) + 1 f(1, x_2, \dots, x_n) \\ &= f(1, x_2, \dots, x_n) \end{aligned}$$

LUT: Look up Table

- LUT is a RAM with data width of 1bit.
- The contents are programmed at power up


Required Function

 

Truth Table


a	b	c	y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Programmed LUT

 


Example: 4-input AND gate

A	B	C	D	O
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

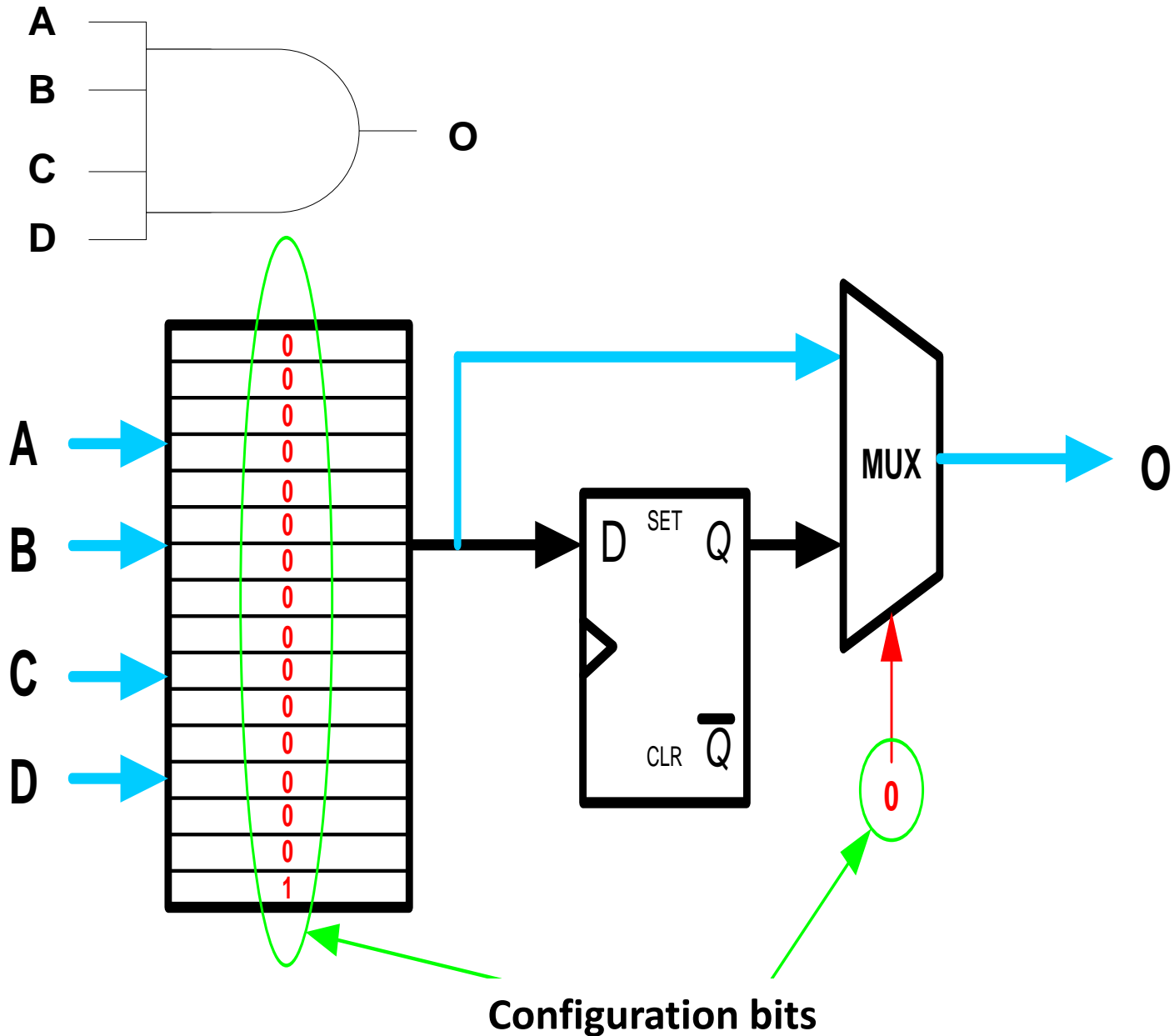

FPGA - Field Programmable Gate Array

 - Programmable logic blocks or CLB
 - (Logic Element “LE”)
 - Implement combinatorial and sequential logic.
Based on LUT and DFF.



FPGA - Field Programmable Gate Array

- Programmable logic blocks (Logic Element “LE”) or CLB
 - Implement combinatorial and sequential logic. Based on LUT and DFF.
- Programmable I/O blocks
 - Configurable I/Os for external connections supports various voltages and tri-states.
- Programmable interconnect
 - Wires to connect inputs , outputs and logic blocks.
 - Clocks
 - short distance local connections
 - long distance connections across chip


FPGA - Field Programmable Gate Array



Logic block



Interconnection switches

 

Field-Programmable Gate Arrays structure

- **Logic blocks**

- To implement combinational and sequential logic

- **Interconnect**


- Wires to connect inputs and outputs to logic blocks

- **I/O blocks**



- Special logic blocks at periphery of device for external connections

- **Key questions:**

 
- How to make logic blocks programmable?
- How to connect the wires?




FPGA structure

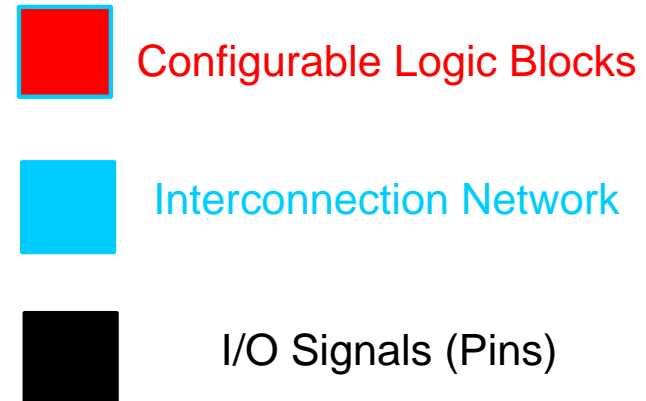 


Simplified CLB Structure

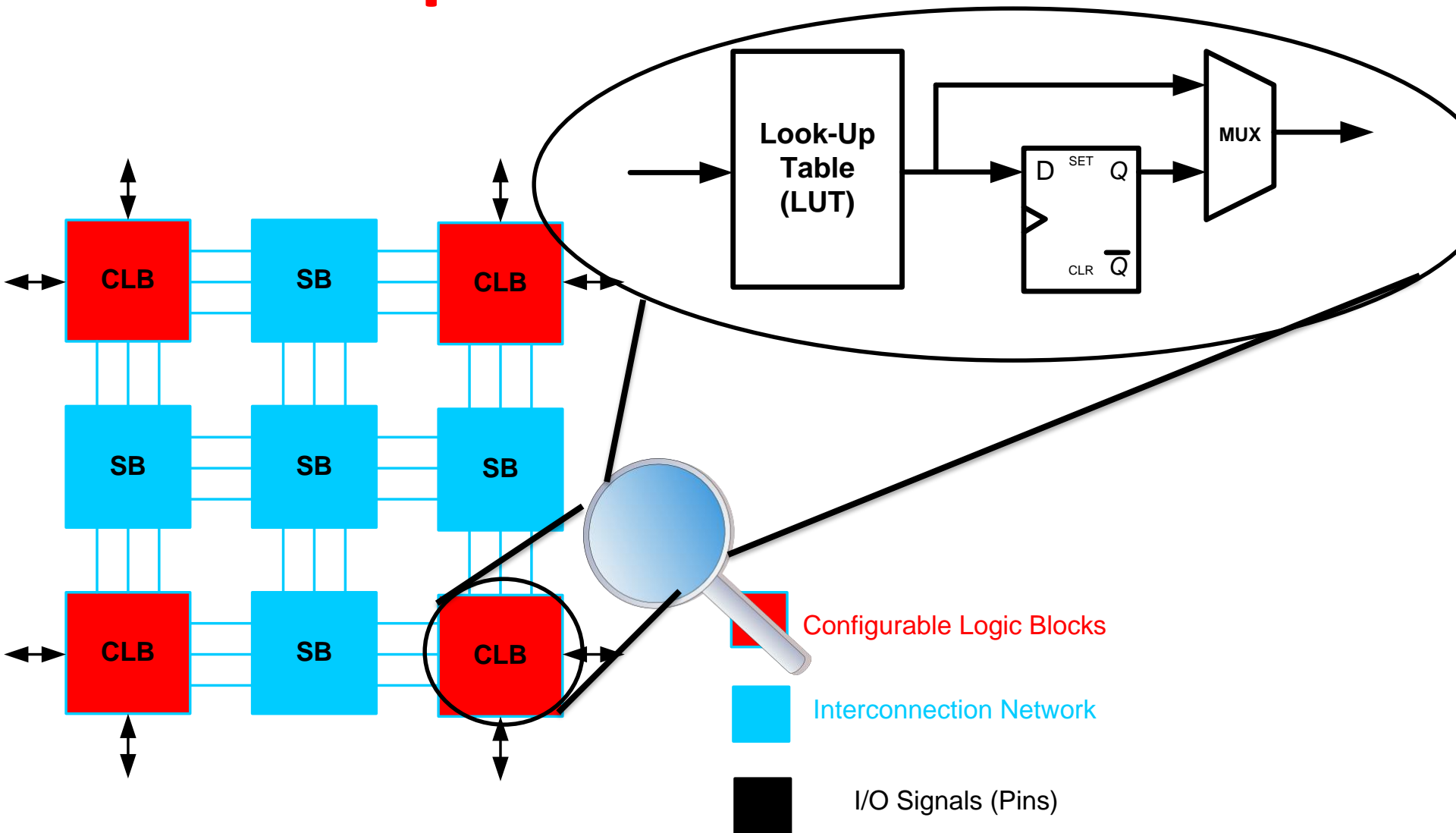


Interconnection Network

 




Configurable Interconnect

 

Placement: Select CLBs

 

Routing: Select path

   

FPGA Advantages

- **Designing with FPGA: Faster, Cheaper**
- **Ideal for customized designs**
 - Product differentiation in a fast-changing market
- **Offer the advantages of high integration**
 - High complexity, density, reliability
 - Low cost, power consumption, small phy. size
- **Avoid the problems of ASICs**
 - high NRE cost, long delay in design and testing
 - increasingly demanding electrical issues

FPGA Advantages

- **Very fast custom logic**
 - massively parallel operation
- **Faster than micro-controllers/and processors**
 - much faster than DSP engines
- **More flexible than dedicated chipsets**
 - allows unlimited product differentiation
- **More affordable and less risky than ASICs**
 - no NRE, min order size, or inventory risk
- **Reprogrammable at any time**
 - in design, in manufacturing, after installation

User Expectations

- **Logic capacity at reasonable cost**
 - 100,000 to a several million gates
 - On-chip fast RAM
- **Clock speed**
 - 150 MHz and above, global clocks, clock management
- **Versatile I/O**
 - To accommodate a variety of standards
- **Design effort and time**
 - synthesis, fast compile times, tested and proven cores
- **Power consumption**
 - must stay within reasonable limits

Field Programmable Device

- **Basic Section of FPD:**
 - Logical Block
 - Routing (Switch Matrix)
 - Input Output Block
- **More Advanced FPD Contains:**
 - On-chip Memory
 - Embedded Processor
 - Clock Management
 - High-Speed Transceiver


Special FPGA functions

- Internal SRAM
- Embedded Multipliers and DSP blocks
- Embedded logic analyzer
- **Embedded CPUs**
- High speed I/O (~10GHz)
- DDR/DDRII/DDRIII SDRAM interfaces
- PLLs

Digilent Xilinx Atlys FPGA Board

- [Xilinx Spartan-6](#) LX45 FPGA,
- 6,822 slices : four 6-input LUTs and eight flip-flops
- 2.1Mbits of block RAM, 128 MB DDR2
- 58 DSP slices
- JTAG programming , RJ-45 Ethernet port
- 4 HDMI video ports
- AC-97 Audio Codec mic, & headphone
- Two on-board USB2
- USB-UART and USB-HID port
- GPIO includes 8 LEDs, 6 buttons, and 8 slide switches

Digilent Xilinx Atlys FPGA Board

 

Digilent Xilinx Basys 3 FPGA Board

- [Xilinx Artix-7 FPGA](#)
- 33,280 logic cells in 5200 slices (four 6-input LUTs and 8 flip-flops)
1,800 Kbits of fast block RAM
- 90 DSP slices
- ADC, USB-JTAG port, USB-UART Bridge , 12-bit VGA output
- USB HID Host for mice, keyboards
- 16 user switches, 16 user LEDs, 5 user pushbuttons , 4-digit 7-segment display


Digilent Xilinx Basys 3 FPGA Board



Digilent Xilinx Zybo FPGA Board

- [Xilinx Zynq-7000 \(XC7Z010-1CLG400C\)](#)
- 28,000 logic cells
- 240 KB Block RAM
- 80 DSP slices , Dual channel, 12-bit, ADC
- **650 MHz dual-core Cortex™-A9 processor**
- JTAG programming and UART to USB converter
- 1G Ethernet, USB 2.0, SDIO, SPI, UART, I2C
- Dual-role HDMI port , VGA port, Ethernet PHY
- OTG USB 2.0 PHY (supports host and device)
- GPIO: 6 pushbuttons, 4 slide switches, 5 LEDs

Digilent Xilinx ZYBO FPGA Board

 

FPGA Design flow

