

CS221: Digital Design

Sequential Design Based on Mealy FSM

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

Outline

- FSM Types : Mealy Machine, Moore Machine
 - Till now we studied Moore Machine
- Example of Mealy Machine
- Comparison of Mealy Vs Moore FSM

FSM Types

- Two main types of FSMs
 - Moore FSM : output is only function of state
 - Mealy FSM: output is function of state and inputs

Set Theoretic Description

Moore Machine is an ordered quintuple

$$M = (S, I, O, \delta, \lambda)$$

where

S = Finite set of states $\neq \Phi, \{s_1, s_2, \dots, s_n\}$

I = Finite set of inputs $\neq \Phi, \{i_1, i_2, \dots, i_m\}$

O = Finite set of outputs $\neq \Phi, \{o_1, o_2, \dots, o_l\}$

δ = Next state function which maps $S \times I \rightarrow S$

λ = Output function which maps $S \rightarrow O$

Set Theoretic Description

Mealy Machine is an ordered quintuple

$$\text{Mealy} = (\mathbf{S}, \mathbf{I}, \mathbf{O}, \delta, \beta)$$

where

\mathbf{S} = Finite set of states $\neq \Phi, \{s_1, s_2, \dots, s_n\}$

\mathbf{I} = Finite set of inputs $\neq \Phi, \{i_1, i_2, \dots, i_m\}$

\mathbf{O} = Finite set of outputs $\neq \Phi, \{o_1, o_2, \dots, o_l\}$

δ = Next state function which maps $\mathbf{S} \times \mathbf{I} \rightarrow \mathbf{S}$

β = Output function which maps $\mathbf{S} \times \mathbf{I} \rightarrow \mathbf{O}$


Clocked synchronous FSM

- **Clocked**
 - All storage elements employ a clock input (i.e. all storage elements are flip-flops)
- **Synchronous**
 - All of the flip flops use the same clock signal

Clocked synchronous FSM

- **FSM**
 - State machine is simply another name for sequential circuits. Finite refers to the fact that the number of states the circuit can assume is finite
- **Async FSM:** A synchronous clocked FSM changes state only when a triggering edge (or tick) occurs on the clock signal


Moore machine

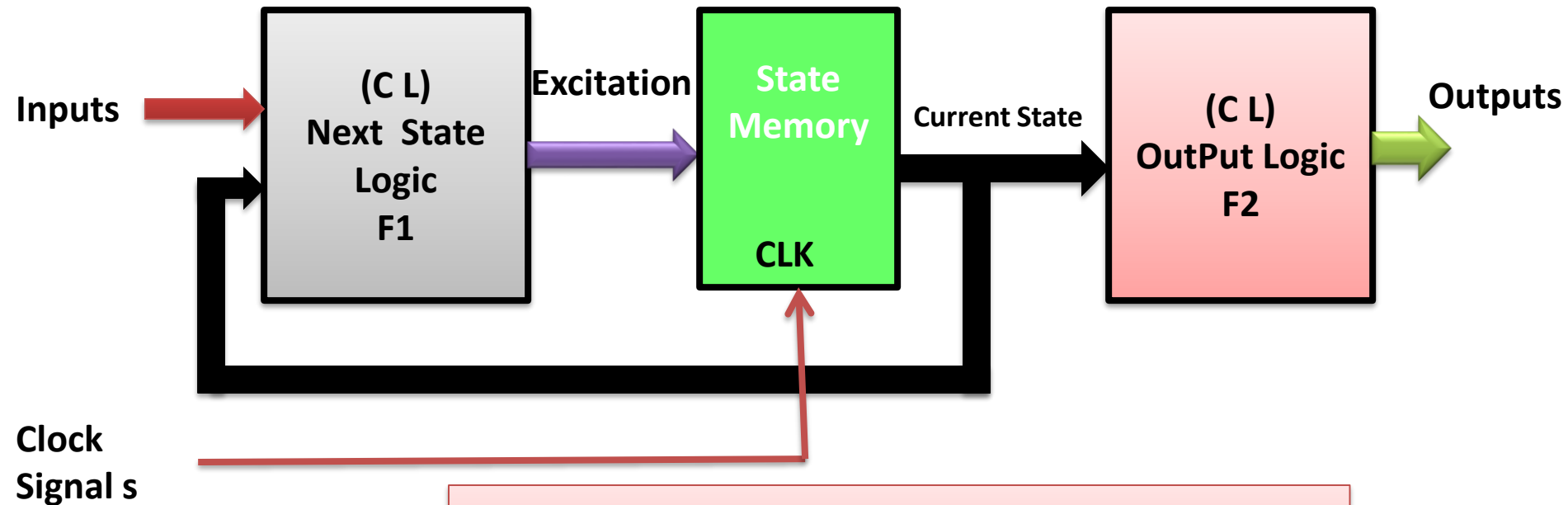

Next state = $F_1(\text{current state, inputs})$
Output = $F_2(\text{current state})$

Mealy machine

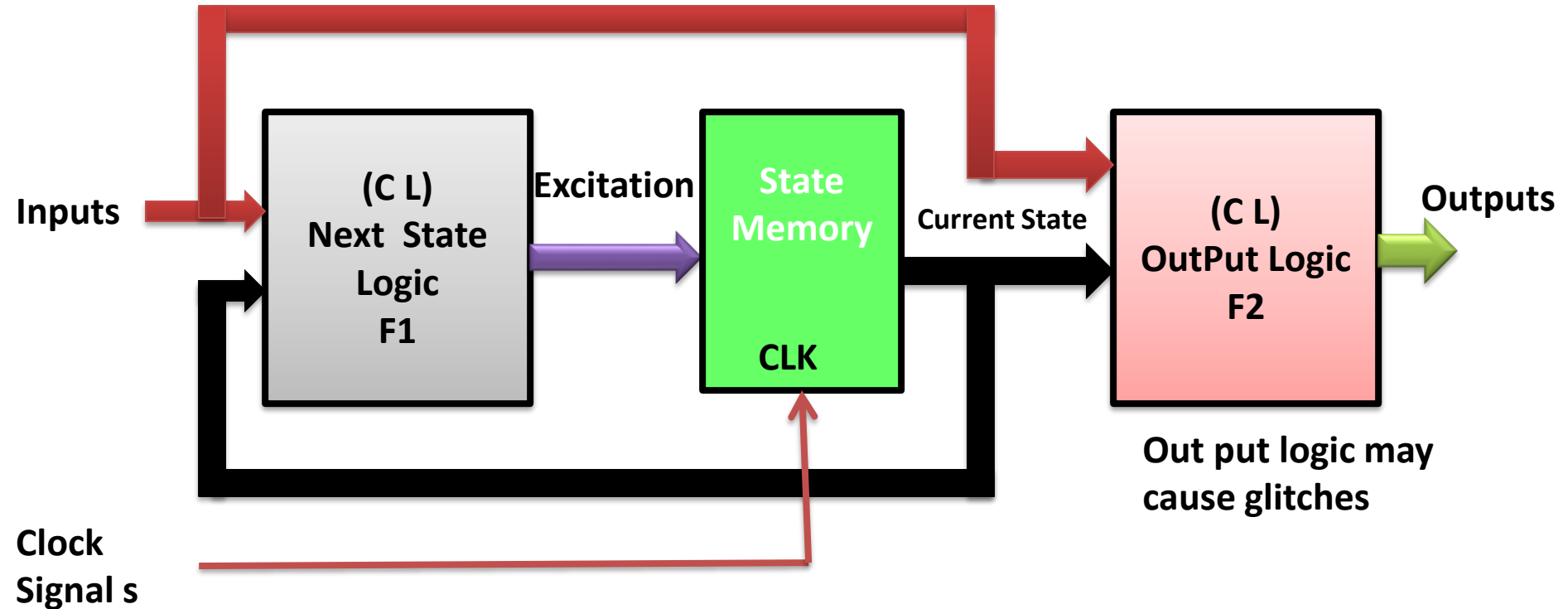- A Much better name of State “Memory” is State Storage




State Storage= Set of n FFs
 2^n State can be stored

Next state = $F_1(\text{current state, inputs})$
Output = $F_2(\text{current state, inputs})$


Mealy machine

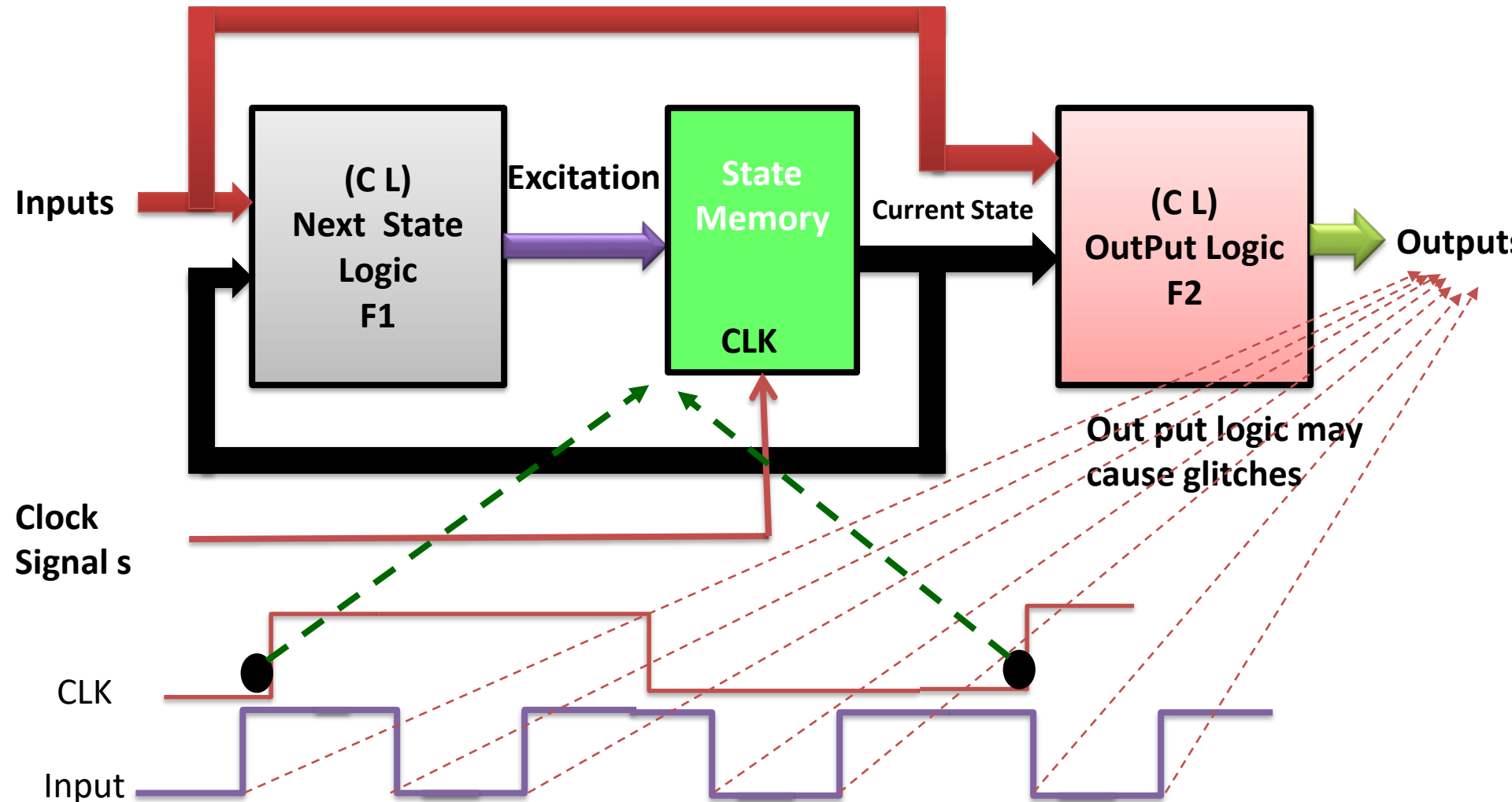- State change VS Output change: State at Clk^\wedge , Output change whenever input changes



Moore FSM : Parity Encoder

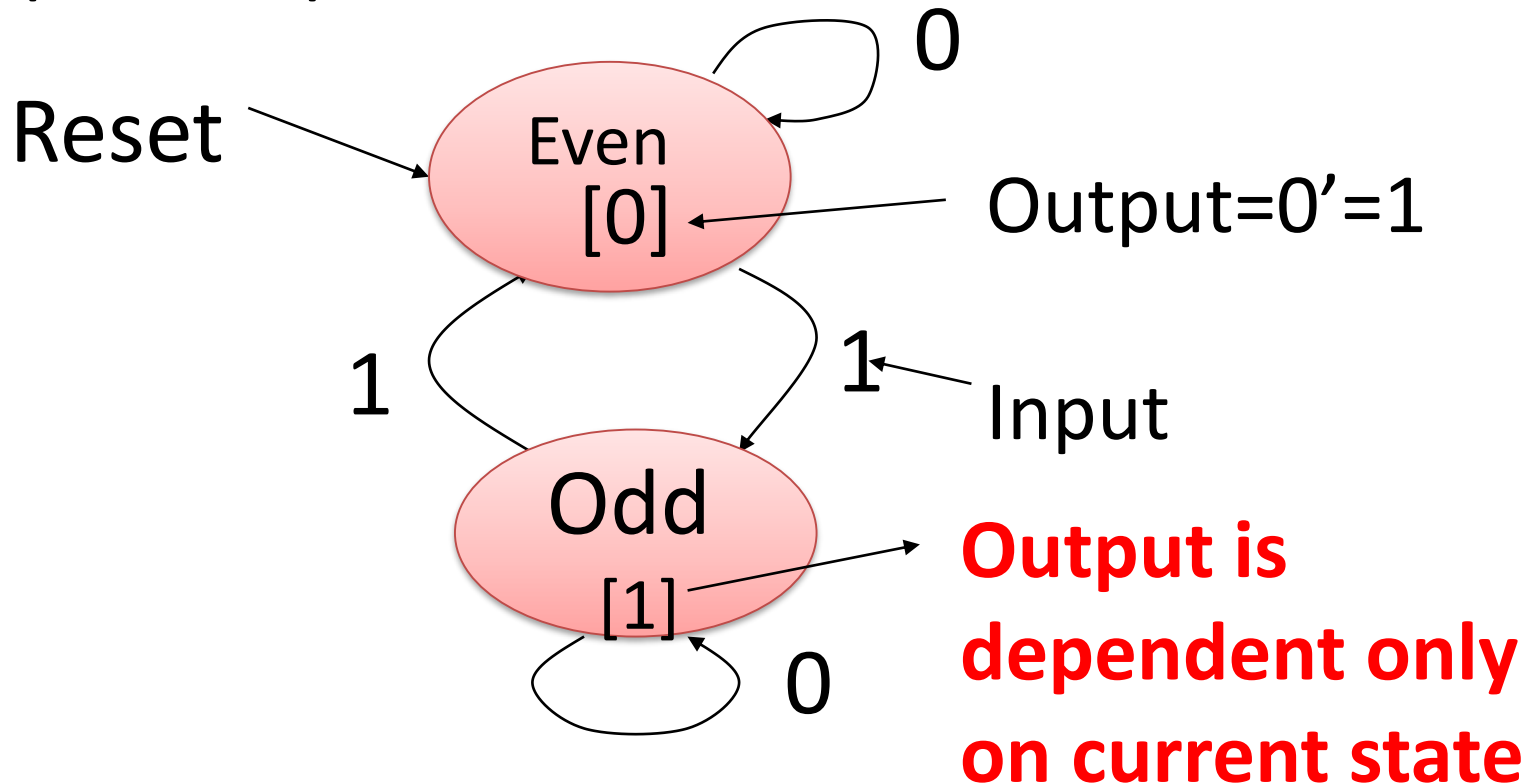
- Input: 1 or 0 // entering as stream
- Output: output a 1 when total number of 1 is even



Output is associated with the state and hence appears after the state transition take place.



Example of Moore & Mealy Machine

- Parity Checker Solution: (Mealy)

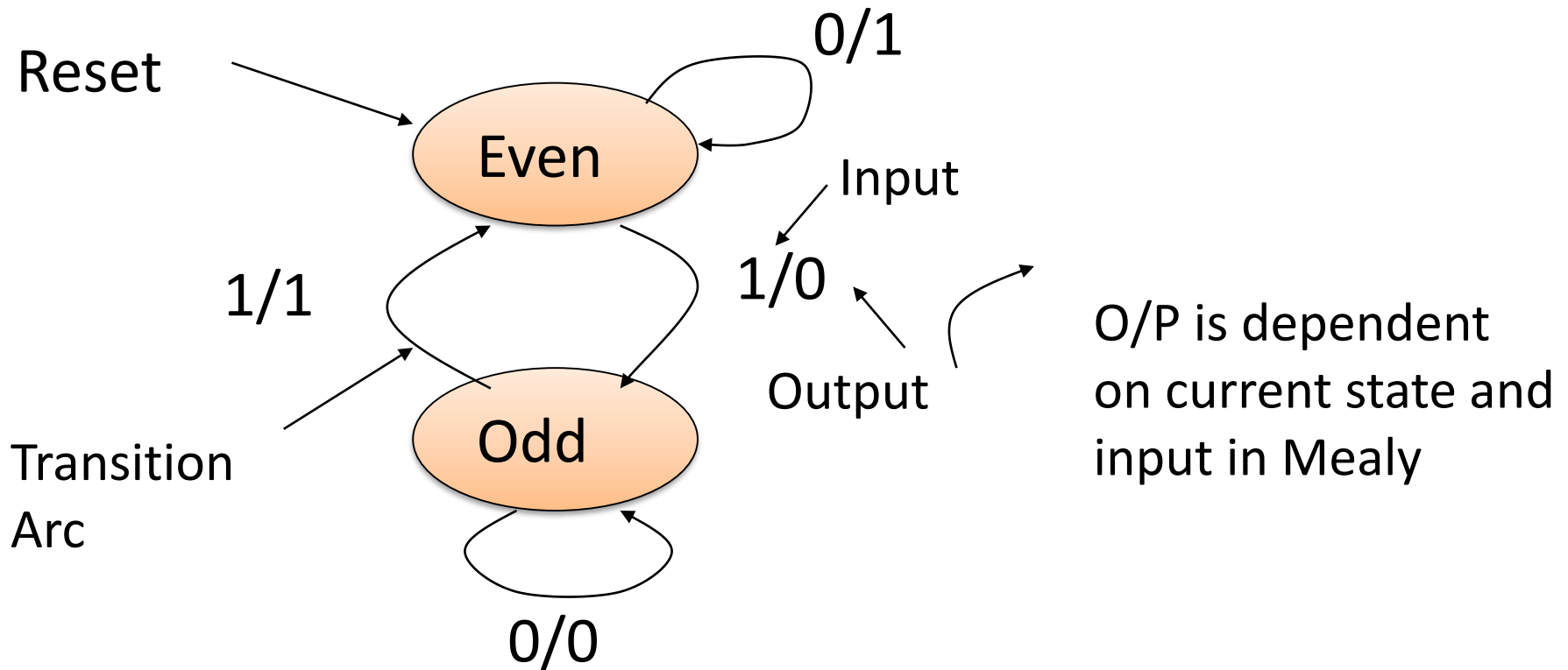


Mealy Machine: Output is associated with the state transition, and appears before the state transition is completed (by the next clock pulse).

Parity Checker: Moore M/C Implementation

  


Moore O/P is synchronized with clock.

Parity Checker: Mealy M/C Implementation

 

D-FF

 

T-FF

Mealy O/P is not synchronized with clock.

Comparison : Mealy FSM Vs Moore FSM

- **Mealy** machines have **less states**
 - Outputs are on transitions ($S \times I$) rather than states (n)
- **Moore** machines are **safer** to use
 - Outputs change at clock edge (always one cycle later)
- Mealy machines: input change can cause output change as soon as logic is done
 - A **big problem** when two machines are interconnected
 - Asynchronous feedback **may** occur if one isn't careful

Comparison : Mealy FSM Vs Moore FSM


- **Mealy** machines **react faster** to inputs
 - react in same cycle – don't need to wait for clock
 - outputs **may** be considerably shorter than the clock cycle
 - in Moore machines, more logic **may** be necessary to decode state into outputs – there **may** be more gate delays after clock edge

FSM Example : Mealy vs Moore

- Design a system that outputs a '1' whenever it receives a multiple of 3 # of 1's (i.e., 0, 3, 6, 9, etc. # of 1's) on a serial input line x.

FSM Example: Moore Machine

 
- Design a system that outputs a '1' whenever it receives a multiple of 3 # of 1's (i.e., 0, 3, 6, 9, etc. # of 1's) on a serial input line x.



Moore Machine

FSM Example: Moore Machine

 - Design a system that outputs a '1' whenever it receives a multiple of 3 # of 1's (i.e., 0, 3, 6, 9, etc. # of 1's) on a serial input line x.



Mealy Machine


Mealy Vs Moore : Problem

- $\Sigma_o = \{t, f\}$ $\Sigma_I = \{0, 1\}$
- Outputs $t \Leftrightarrow$ at least 2 last input digits are same

Solutions to Problem

- Mealy implementation
 - Needs only 3 states
- Moore implementation
 - Needs 2 more almost duplicated states just in order to the output value t there.

FSM: Mealy Machine

 


FSM: Moore Machine

Outputs **true** if at least 2 last input digits are same

Is it possible to design Moore
FSM of the same problem with
3 state ?

You can try now..

FSM: Moore Machine

 

Next Class: FSM Optimization

- How to reduce the number of states in a FSM if it is specified with redundant states.
- Both type of FSM will be used
 - Some Examples are with Moore FSM
 - Some Examples are with Mealy FSM