

**CS221: Digital Design**

# **Finite State Machine**

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

# Outline

- Finite State Machine
- Formal definition
- FSM implementation
- FSM Examples

# Combinational Circuit

- Can you formally model all the combinational circuit using Boolean Algebra?



YES

# Sequential Circuit: FSM


- Combinational Circuit : Formal Approach
  - Boolean Algebra
  - Circuit Minimization (K-Map, Quine McCluskey, Espresso...)
- Sequential Circuit : Formal Approach
  - Finite State Machine

**Formally Describe/mathematically Describe**

Boolean Algebra: Working Combinational Circuit

Finite State Machine: Working of Sequential Circuit

# Sequential Circuit: FSM

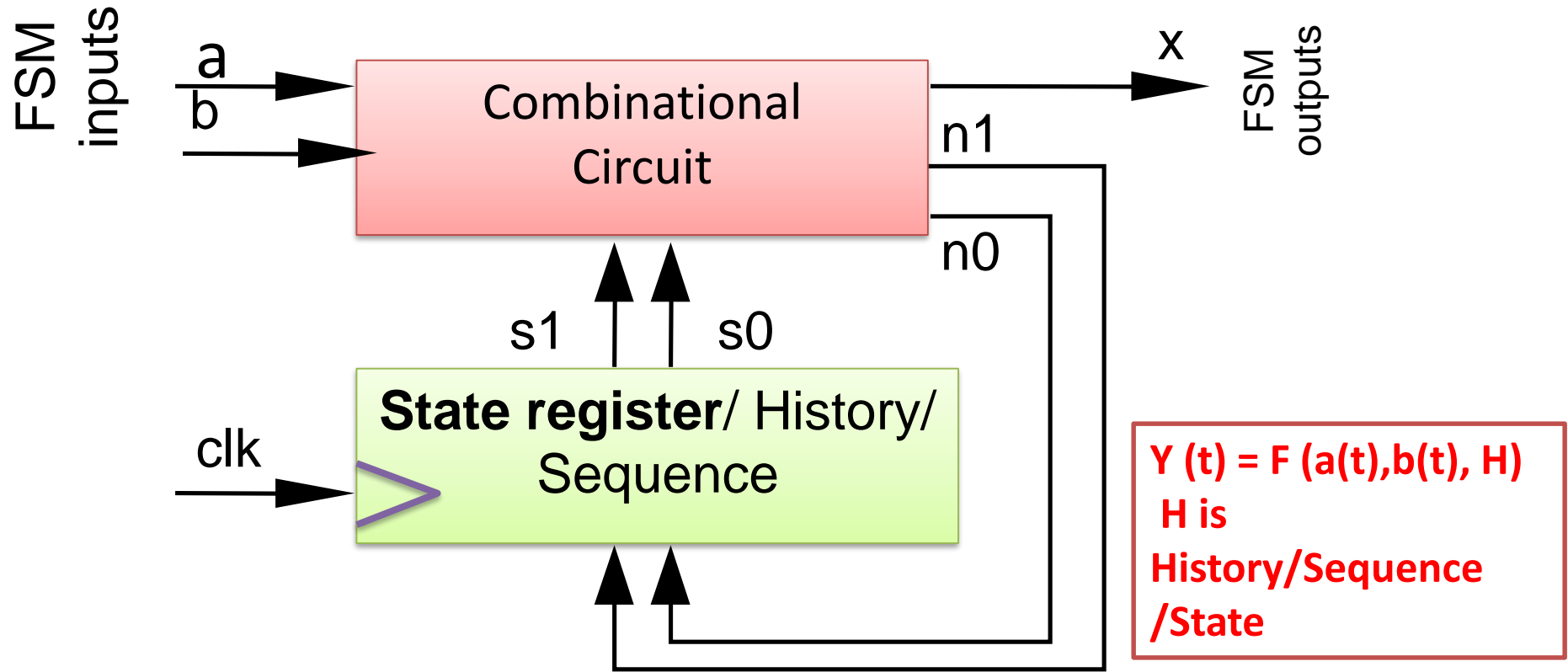

Formally Describe/mathematically Describe

Boolean Algebra: Working Combinational Circuit

Finite State Machine: Working of Sequential Circuit

# Already Designed Sequential Circuit

- Flip Flops ( RS, JK, T, D)
- Register (Shift, PIPO), Memory
- Counter : Async, Sync, Modulo Counter
- Counter using Shift register

Till now we have not used  
formal approach to design  
these

# Need a Better Way to Design Sequential Circuits

- Combinational circuit design process had two important things
  1. A formal way to describe desired circuit behavior
    - Boolean equation, or truth table
  2. A well-defined process to convert that behavior to a circuit
- We need those things for sequence circuit design

# Sequential Circuit

- Can we model all synchronous sequential circuit using some model?

Yes, with Finite  
State Machine  
(FSM)



# Finite State Machine

- Finite-State Machine (FSM)
  - A way to describe desired behavior of sequential circuit
  - Similar/Akin to Boolean equations for combinational behavior
  - List states, and transitions among states

# Set Theoretic Description

Moore Machine is an ordered quintuple

$$M = (S, I, O, \delta, \lambda)$$

where

$S$  = Finite set of states  $\neq \Phi, \{s_1, s_2, \dots, s_n\}$

$I$  = Finite set of inputs  $\neq \Phi, \{i_1, i_2, \dots, i_m\}$

$O$  = Finite set of outputs  $\neq \Phi, \{o_1, o_2, \dots, o_l\}$

$\delta$  = Next state function which maps  $S \times I \rightarrow S$

$\lambda$  = Output function which maps  $S \rightarrow O$

# Clocked synchronous FSM


- **Clocked**
  - All storage elements employ a clock input (i.e. all storage elements are flip-flops)
- **Synchronous**
  - All of the flip flops use the same clock signal

# Clocked Asynchronous FSM


- **FSM**
  - State machine is simply another name for sequential circuits.
  - Finite refers to the fact that the number of states the circuit can assume is finite
- **Async FSM:** A synchronous clocked FSM changes state only when a triggering edge (or tick) occurs on the clock signal
  - **This will not be our focus in this course**
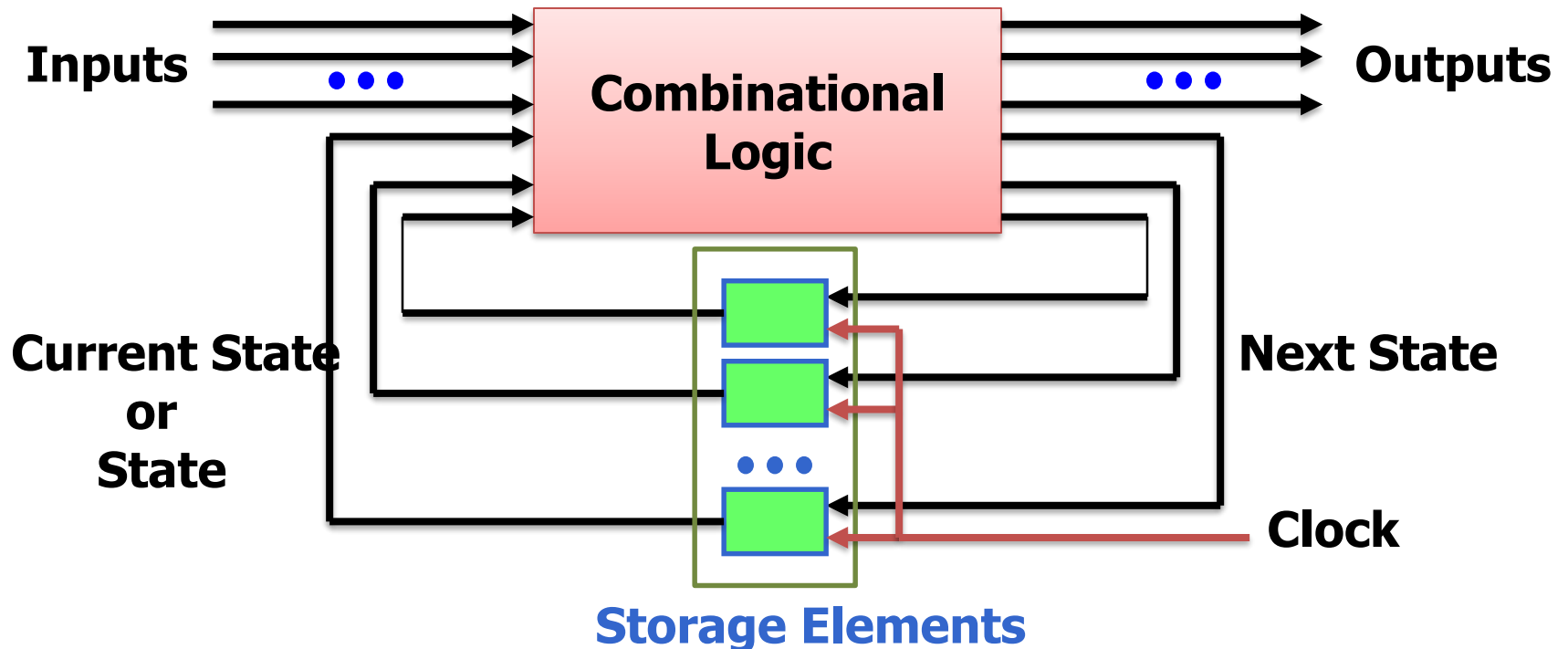
# Clocked synchronous FSM structure

- **States:** determined by possible values in sequential storage elements
- **Transitions:** change of state
- **Clock:** controls when state can change by controlling storage elements



# Moore machine

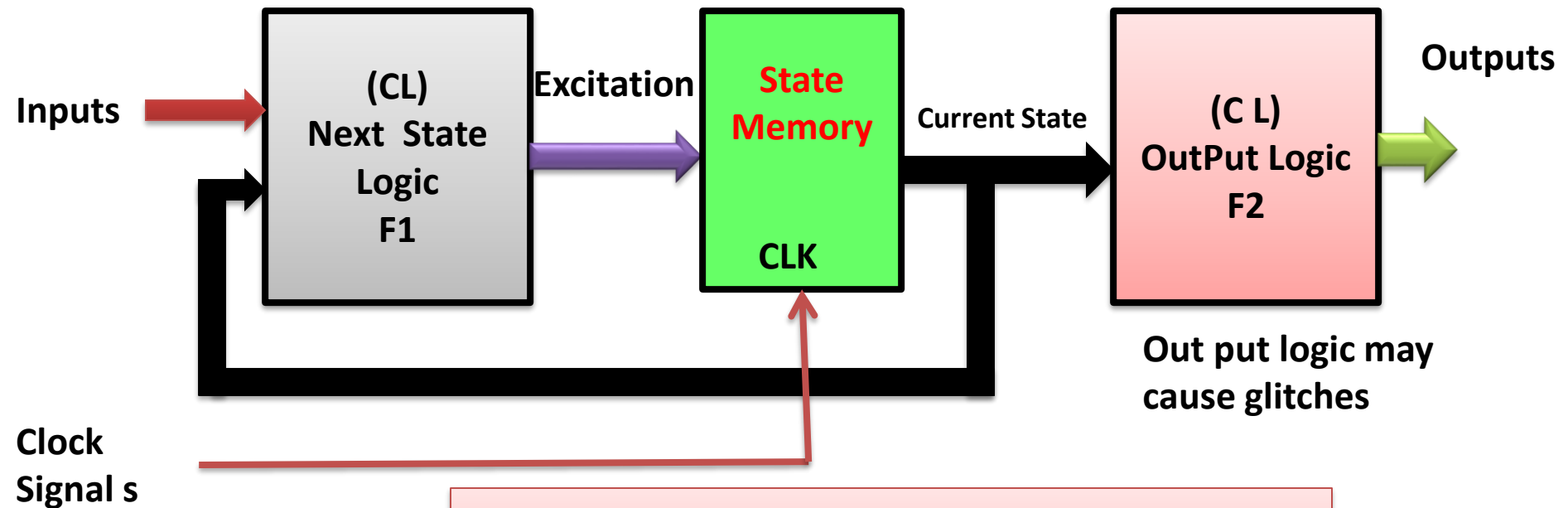

**Next state =  $F_2(\text{current state, inputs})$**   
**Output =  $G_2(\text{current state})$**

# **FSM Example 1**

## **ON-OFF FSM**


# Finite State Machine: Example 1

- **On-off Example FSM**
- Make  $x$  change toggle (0 to 1, or 1 to 0) every clock cycle
- Two states: “Off” ( $x=0$ ), and “On” ( $x=1$ )
- Transition from Off to On, or On to Off, on rising clock edge
- Arrow with no starting state points to initial state (when circuit first starts)



# Finite State Machine: Example

Outputs: x

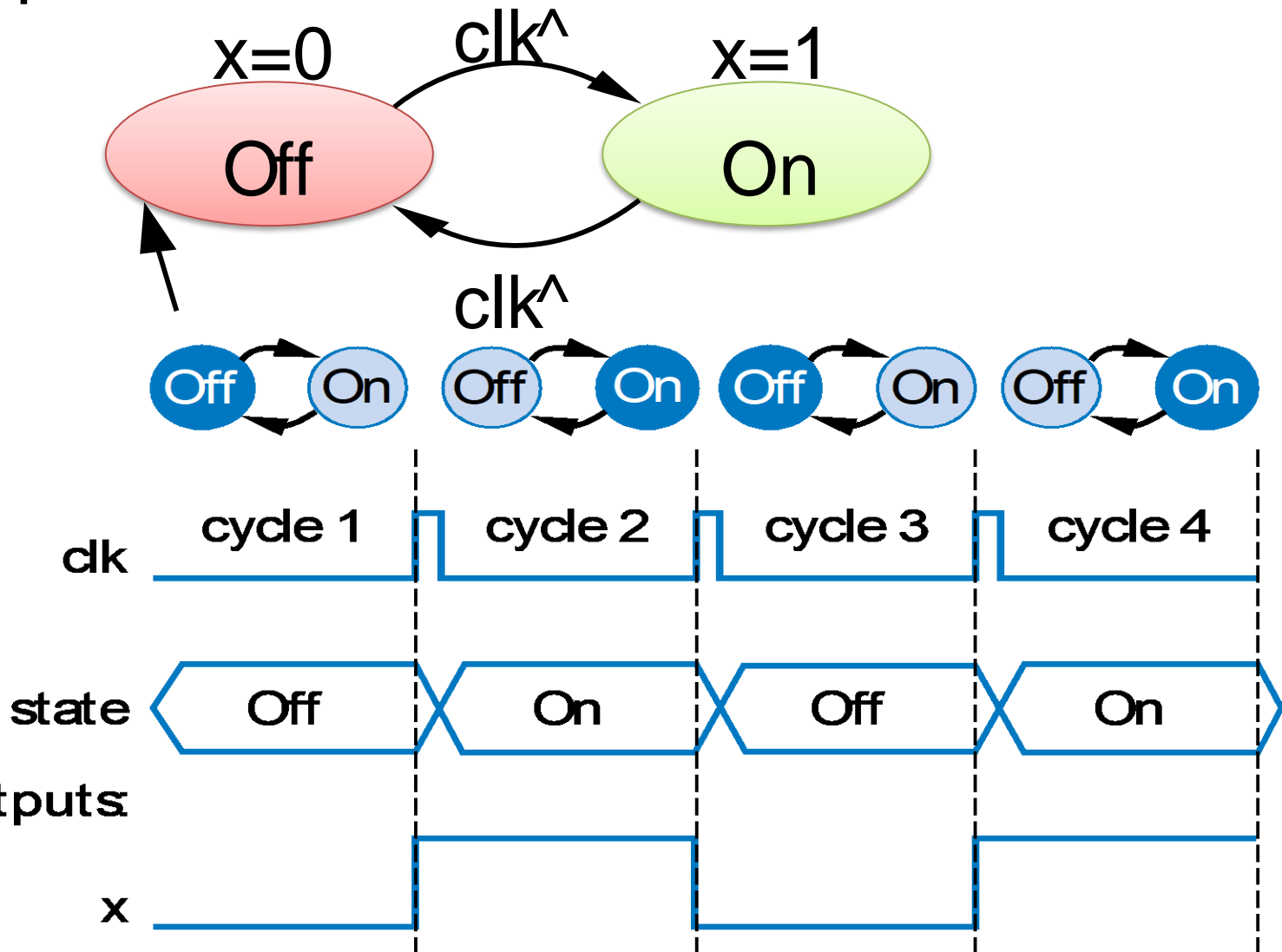

# FSM

We often draw FSM graphically, known as *state diagram*


Can also use table (state table), or textual languages

# FSM Controller for On-Off Example

Input		Output	
CLK	P	X	N
RE 1	0	1	1
RE 1	1	0	0

In this example For simplicity:

 we are using X, N are function of P and CLK But in FSM X is function of P





Think of Clock Enable: only **Rising Edge (RE)**  
Above one may not work: Level Sensitive

# Controller for On-Off

Input		Output	
CLK	P	X	N
RE 1	0	1	1
RE 1	1	0	0


**D-FF used to store the Present state**

 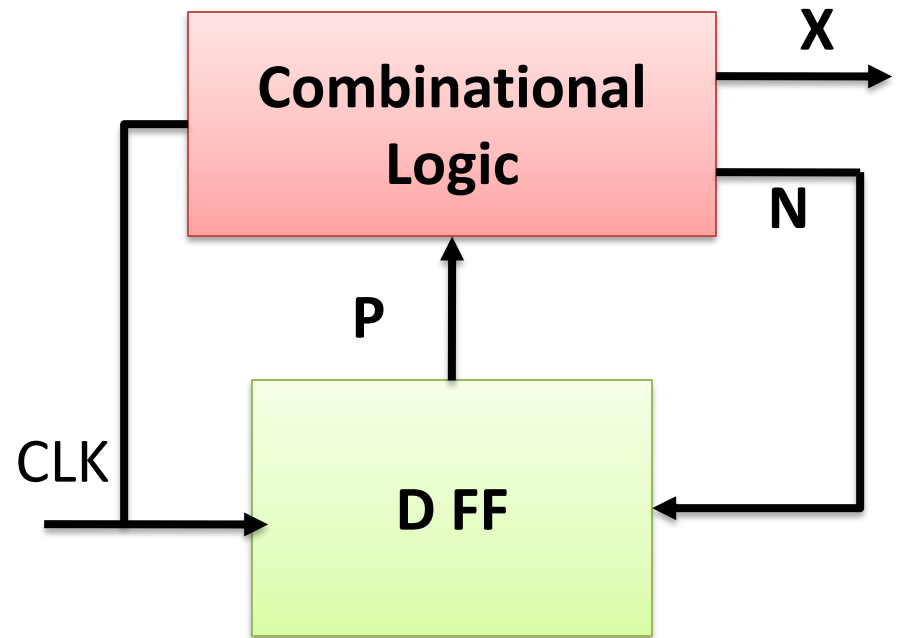

Rising Edge: Clock implicit

# Controller for On-Off

Input		Output	
CLK	P	X	N
RE 1	0	1	1
RE 1	1	0	0

 

This a T-FF design using a D-FF  
Where T is always 1  
== > T is not an external input

Rising Edge: Clock implicit

# **FSM Example 2**

## **D-FF**

# FSM for D-FF


PS= Q(t)	Input	NS =Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

$Q(t+1)=\text{Input}$

State: 0, 1

Input : 0, 1

Output: 0,1

 

# FSM Controller for D-FF is D-FF


$$Q(t+1)=D$$

State: 0, 1

Input : 0, 1

Output: 0,1

PS= Q(t)	Input (D)	NS =Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

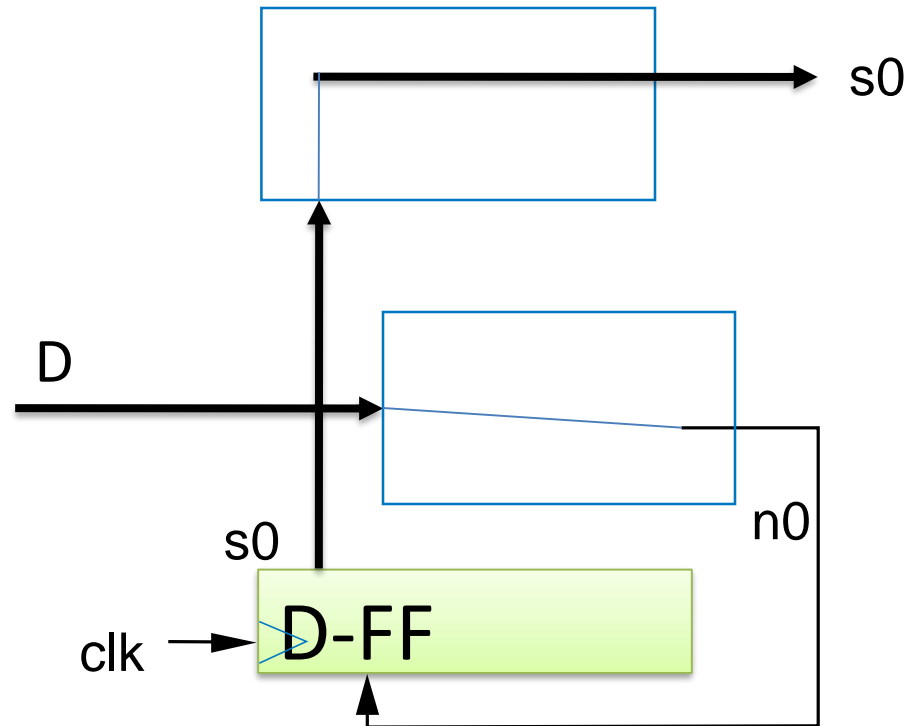



# **FSM Example 3**

## **T-FF**

# FSM for T-FF


PS= Q(t)	Input(T)	NS =Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = Q'(t)T(t) + Q(t)T'(t)$$

**State: 0, 1**

**Input : 0, 1**

**Output: 0,1**

 

# FSM Controller for T-FF


PS= Q(t)	Input	NS =Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = Q'(t)T(t) + Q(t)T'(t)$$

State: 0, 1

Input : 0, 1

Output: 0, 1

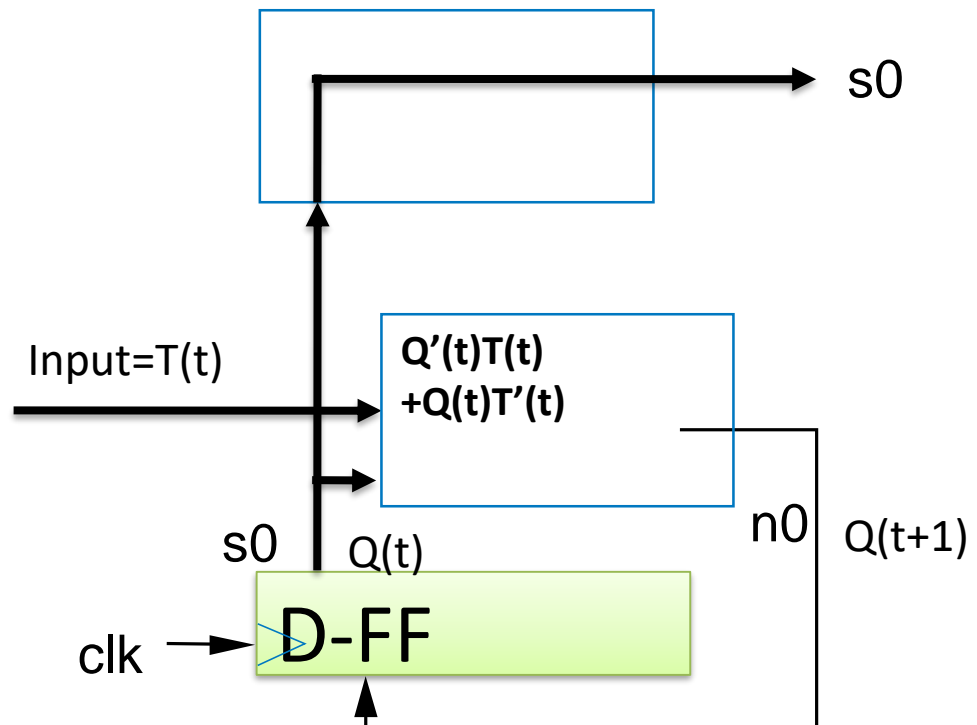

# **FSM Example 4**


## **JK-FF**

# FSM for JK-FF

State: 0, 1

Input : 00, 01, 10, 11

Output: 0, 1

 

# FSM for JK-FF

State: 0, 1

Input : 00, 01,10,11

Output: 0,1

PS= Q(t)	Input(JK)	NS =Q(t+1)
0	00	0
0	01	0
0	10	1
0	11	1
1	00	1
1	01	0
1	10	1
1	11	0

$$Q(t+1)=JQ'(t)+K'Q(t)$$


# FSM Controller for JK-FF

State: 0, 1

Input : 00, 01, 10, 11

Output: 0, 1

$$Q(t+1) = JQ'(t) + K'Q(t)$$

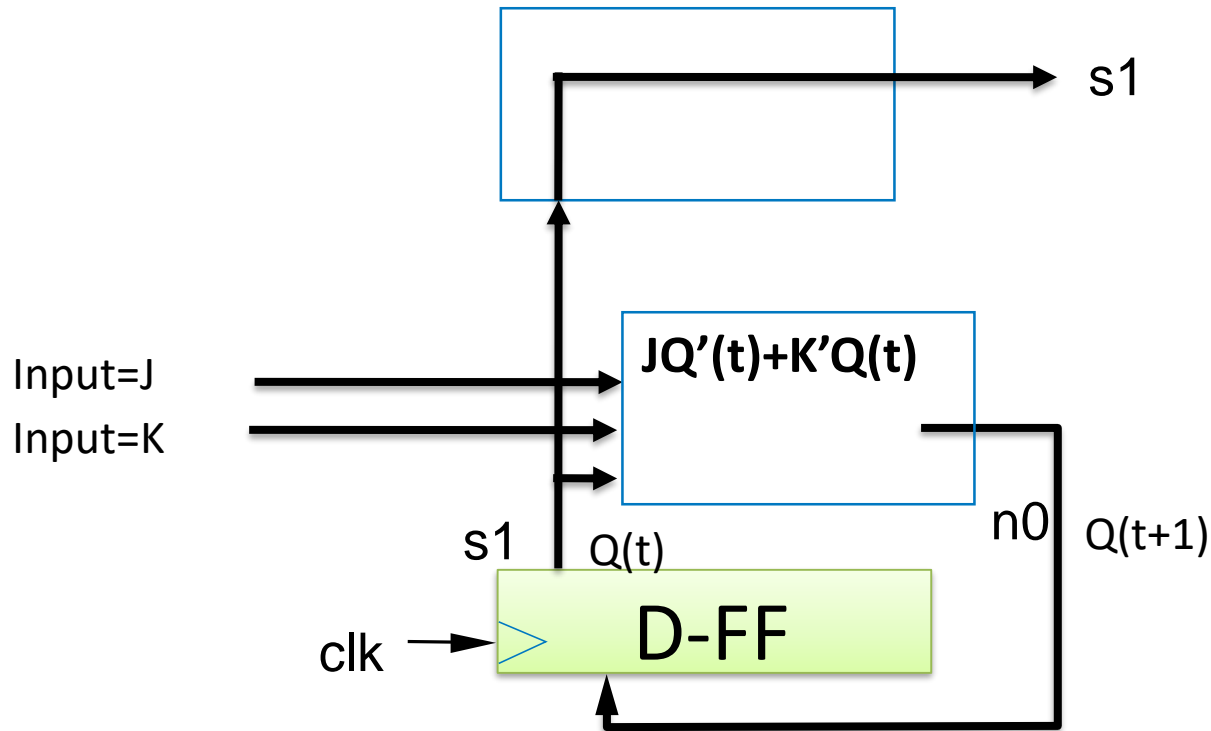

# **FSM Example 5**

## **RS-FF**




# FSM for RS-FF

State: 0, 1

Input : 00, 01,10,11

Output: 0,1

 

# FSM for RS-FF

State: 0, 1

Input : 00, 01,10,11

Output: 0,1

PS= Q(t)	Input(RS)	NS =Q(t+1)
0	00	0
0	01	0
0	10	1
0	11	x
1	00	1
1	01	0
1	10	1
1	11	x

$$Q(t+1)=R+Q(t).S'$$

# FSM Controller for RS-FF

State: 0, 1

$Q(t+1) = R + Q(t) \cdot S'$  Input : 00, 01, 10, 11

Output: 0, 1

